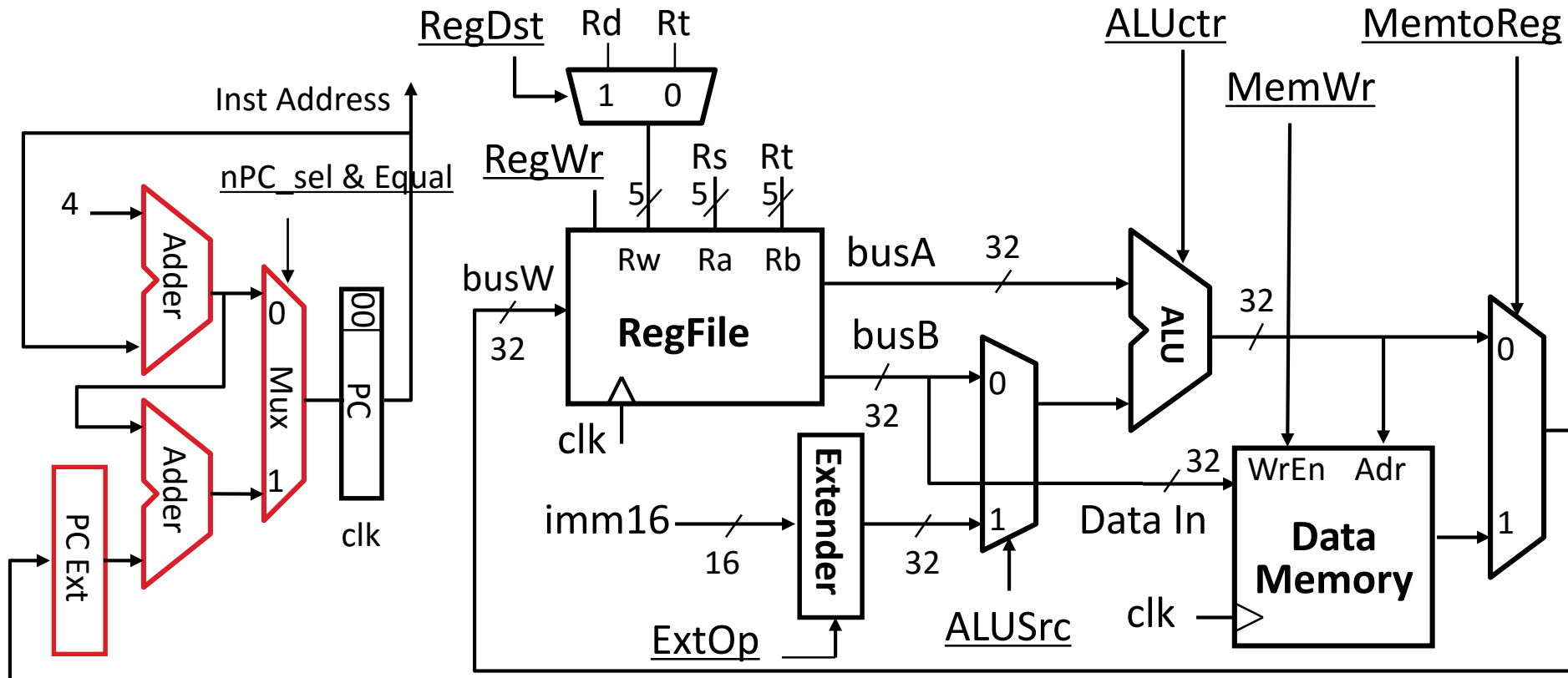



# Datapath Control Signals

- ExtOp: “zero”, “sign”
- ALUsrc: 0  $\Rightarrow$  regB;  
1  $\Rightarrow$  immed
- ALUctr: “ADD”, “SUB”, “OR”


- MemWr: 1  $\Rightarrow$  write memory
- MemtoReg: 0  $\Rightarrow$  ALU; 1  $\Rightarrow$  Mem
- nPC\_sel: 0  $\Rightarrow$  “+4”; 1  $\Rightarrow$  “br”
- RegDst: 0  $\Rightarrow$  “rt”; 1  $\Rightarrow$  “rd”
- RegWr: 1  $\Rightarrow$  write register



# Where Do Control Signals Come From?

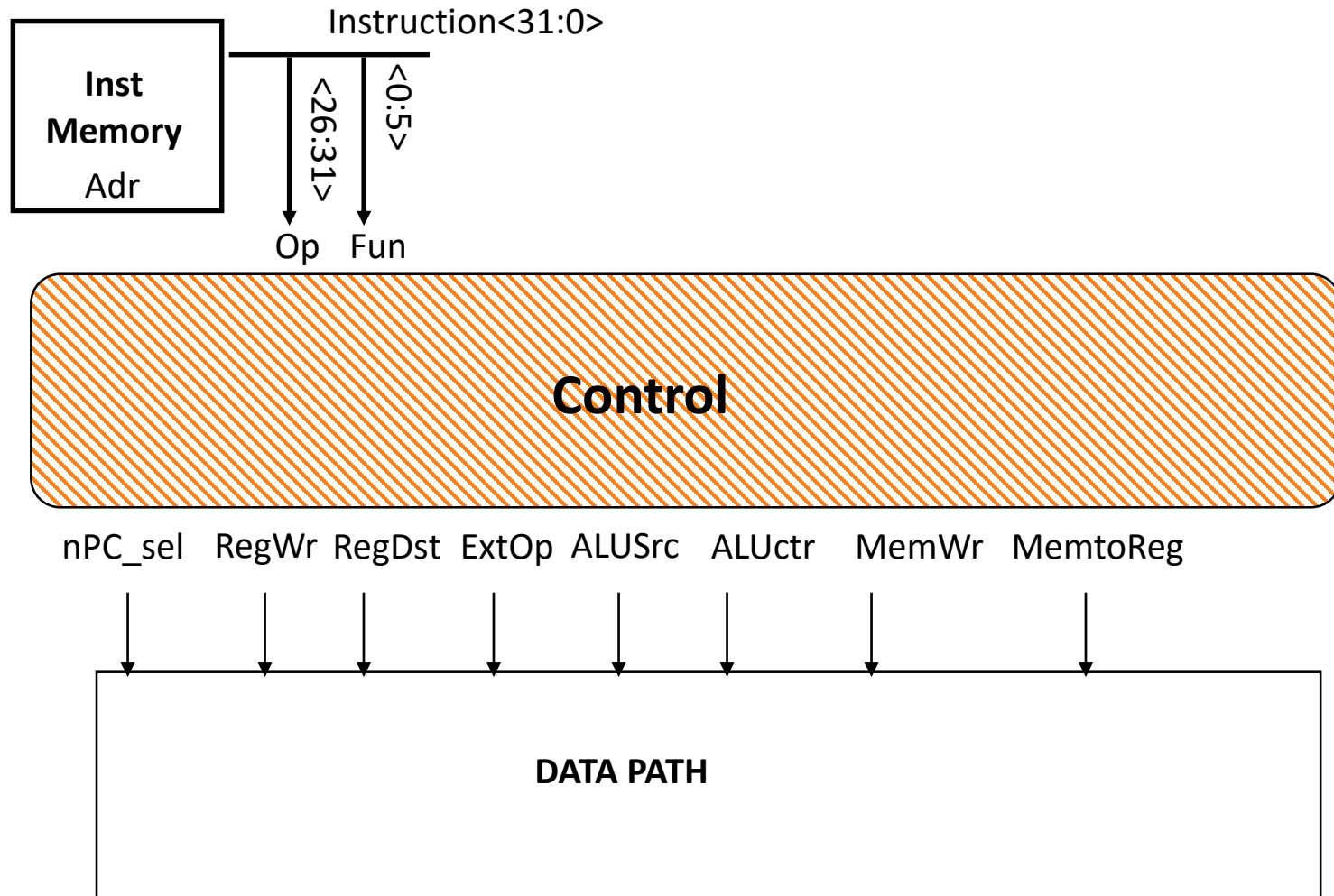

# P&H Figure 4.17

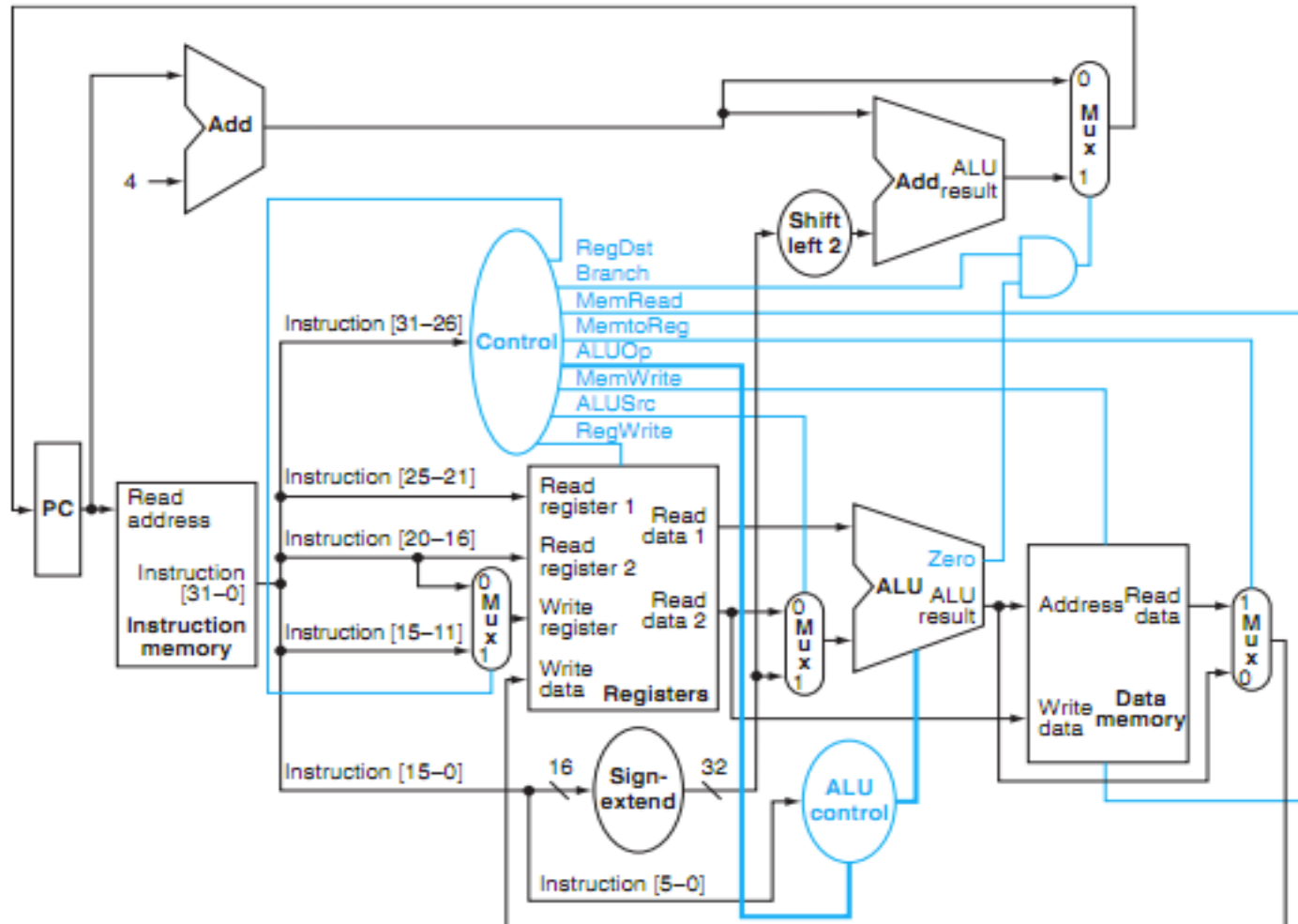

# Summary of the Control Signals (1/2)

<u>inst</u>	<u>Register Transfer</u>
add	$R[rd] \leftarrow R[rs] + R[rt]; PC \leftarrow PC + 4$ $ALUsrc=RegB, ALUctr="ADD", RegDst=rd, RegWr, nPC\_sel="+4"$
sub	$R[rd] \leftarrow R[rs] - R[rt]; PC \leftarrow PC + 4$ $ALUsrc=RegB, ALUctr="SUB", RegDst=rd, RegWr, nPC\_sel="+4"$
ori	$R[rt] \leftarrow R[rs] + zero\_ext(Imm16); PC \leftarrow PC + 4$ $ALUsrc=Im, Extop="Z", ALUctr="OR", RegDst=rt, RegWr, nPC\_sel="+4"$
lw	$R[rt] \leftarrow MEM[ R[rs] + sign\_ext(Imm16)]; PC \leftarrow PC + 4$ $ALUsrc=Im, Extop="sn", ALUctr="ADD", MemtoReg, RegDst=rt, RegWr,$ $nPC\_sel = "+4"$
sw	$MEM[ R[rs] + sign\_ext(Imm16)] \leftarrow R[rs]; PC \leftarrow PC + 4$ $ALUsrc=Im, Extop="sn", ALUctr = "ADD", MemWr, nPC\_sel = "+4"$
beq	if ( $R[rs] == R[rt]$ ) then $PC \leftarrow PC + sign\_ext(Imm16)$    00 else $PC \leftarrow PC + 4$ $nPC\_sel = "br", ALUctr = "SUB"$


# Summary of the Control Signals (2/2)

See Appendix A → **func**  
→ **op**

	10 0000	10 0010	We Don't Care :-)				
	00 0000	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	<b>add</b>	<b>sub</b>	<b>ori</b>	<b>lw</b>	<b>sw</b>	<b>beq</b>	<b>jump</b>
<b>RegDst</b>	1	1	0	0	x	x	x
<b>ALUSrc</b>	0	0	1	1	1	0	x
<b>MemtoReg</b>	0	0	0	1	x	x	x
<b>RegWrite</b>	1	1	1	1	0	0	0
<b>MemWrite</b>	0	0	0	0	1	0	0
<b>nPCsel</b>	0	0	0	0	0	1	?
<b>Jump</b>	0	0	0	0	0	0	1
<b>ExtOp</b>	x	x	0	1	1	x	x
<b>ALUctr&lt;2:0&gt;</b>	Add	Subtract	Or	Add	Add	Subtract	x

	31	26	21	16	11	6	0	
<b>R-type</b>	op	rs	rt	rd	shamt	funct		add, sub
<b>I-type</b>	op	rs	rt	immediate				ori, lw, sw, beq
<b>J-type</b>	op	target address						jump

# Boolean Exprs for Controller

 

Op 0-5 are really Instruction bits 26-31  
 Func 0-5 are really Instruction bits 0-5

$$\text{rtype} = \sim op_5 \bullet \sim op_4 \bullet \sim op_3 \bullet \sim op_2 \bullet \sim op_1 \bullet \sim op_0,$$

$$\text{ori} = \sim op_5 \bullet \sim op_4 \bullet op_3 \bullet op_2 \bullet \sim op_1 \bullet op_0$$

$$\text{lw} = op_5 \bullet \sim op_4 \bullet \sim op_3 \bullet \sim op_2 \bullet op_1 \bullet op_0$$

$$\text{sw} = op_5 \bullet \sim op_4 \bullet op_3 \bullet \sim op_2 \bullet op_1 \bullet op_0$$


$$\text{beq} = \sim op_5 \bullet \sim op_4 \bullet \sim op_3 \bullet op_2 \bullet \sim op_1 \bullet \sim op_0$$

$$\text{jump} = \sim op_5 \bullet \sim op_4 \bullet \sim op_3 \bullet \sim op_2 \bullet op_1 \bullet \sim op_0$$

$$\text{add} = \text{rtype} \bullet func_5 \bullet \sim func_4 \bullet \sim func_3 \bullet \sim func_2 \bullet \sim func_1 \bullet \sim func_0$$

$$\text{sub} = \text{rtype} \bullet func_5 \bullet \sim func_4 \bullet \sim func_3 \bullet \sim func_2 \bullet func_1 \bullet \sim func_0$$

# Controller Implementation

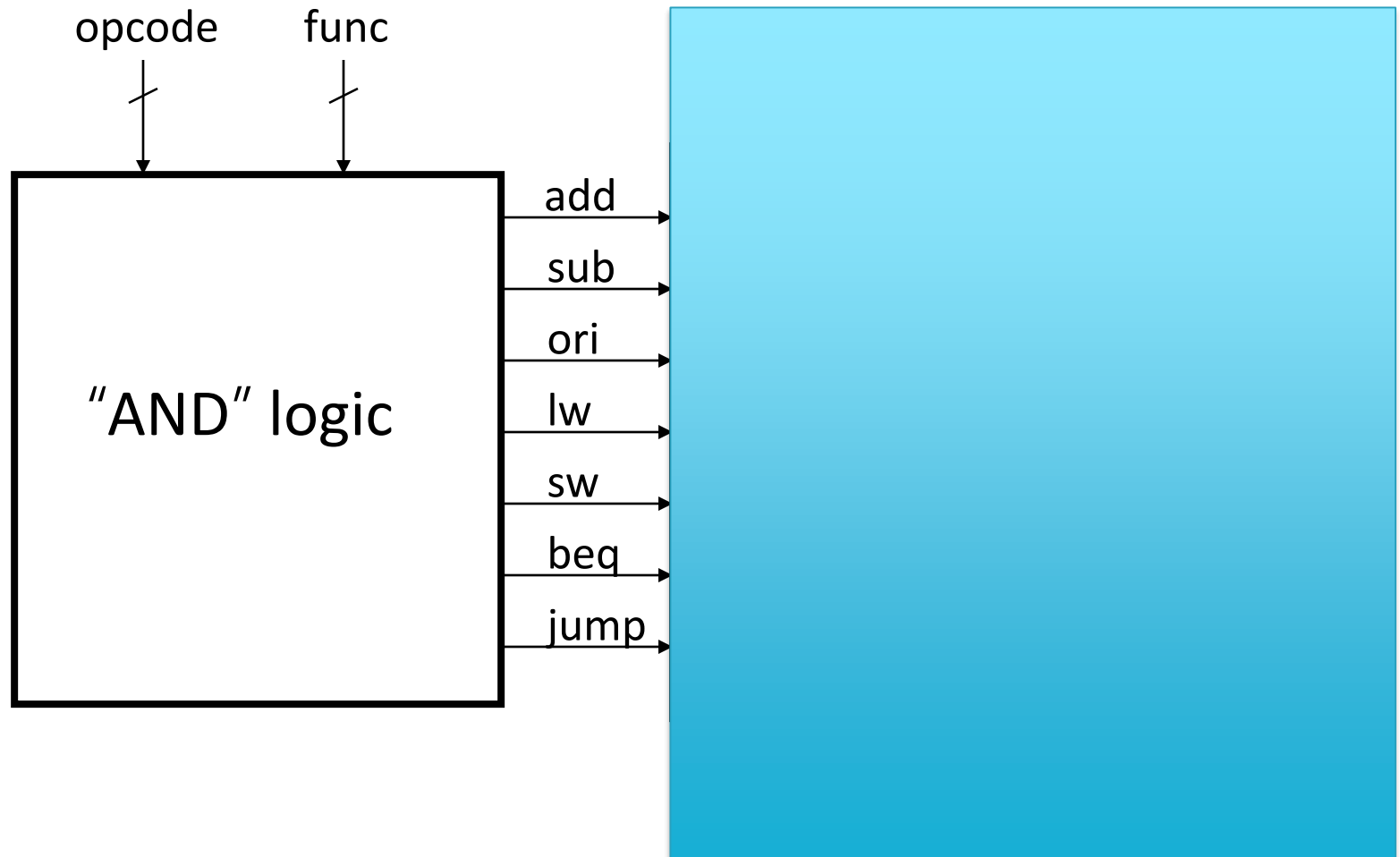

# Boolean Exprs for Controller


```
RegDst      = add + sub
ALUSrc      = ori + lw + sw
MemtoReg    = lw
RegWrite    = add + sub + ori + lw
MemWrite    = sw
nPCsel      = beq
Jump        = jump
ExtOp       = lw + sw
ALUctr[0]   = sub + beq
ALUctr[1]   = ori
```

(assume ALUctr is 00 ADD, 01 SUB, 10 OR)


**How do we implement this in gates?**



# Controller Implementation

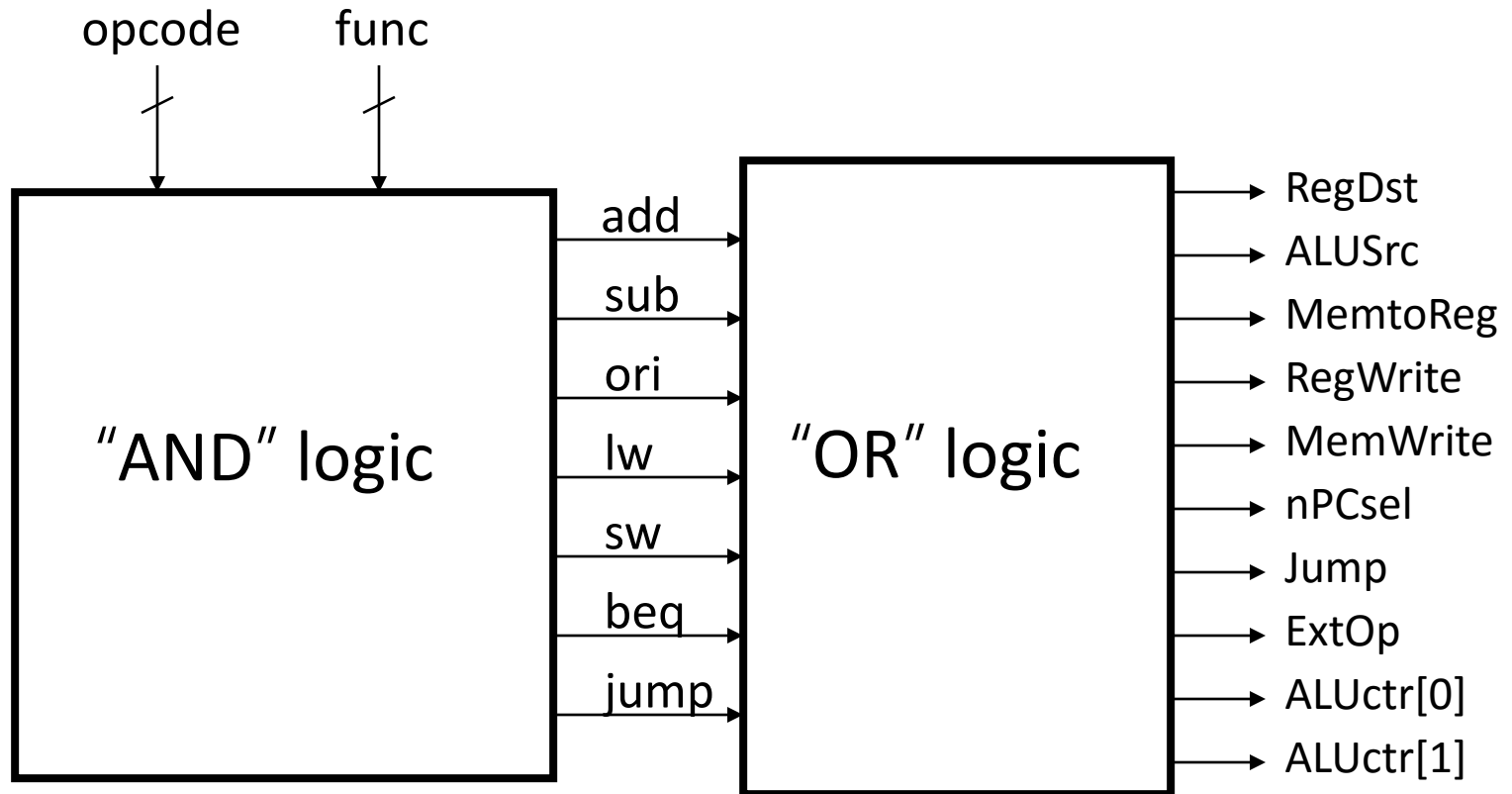


# Call home, we've made HW/SW contact!

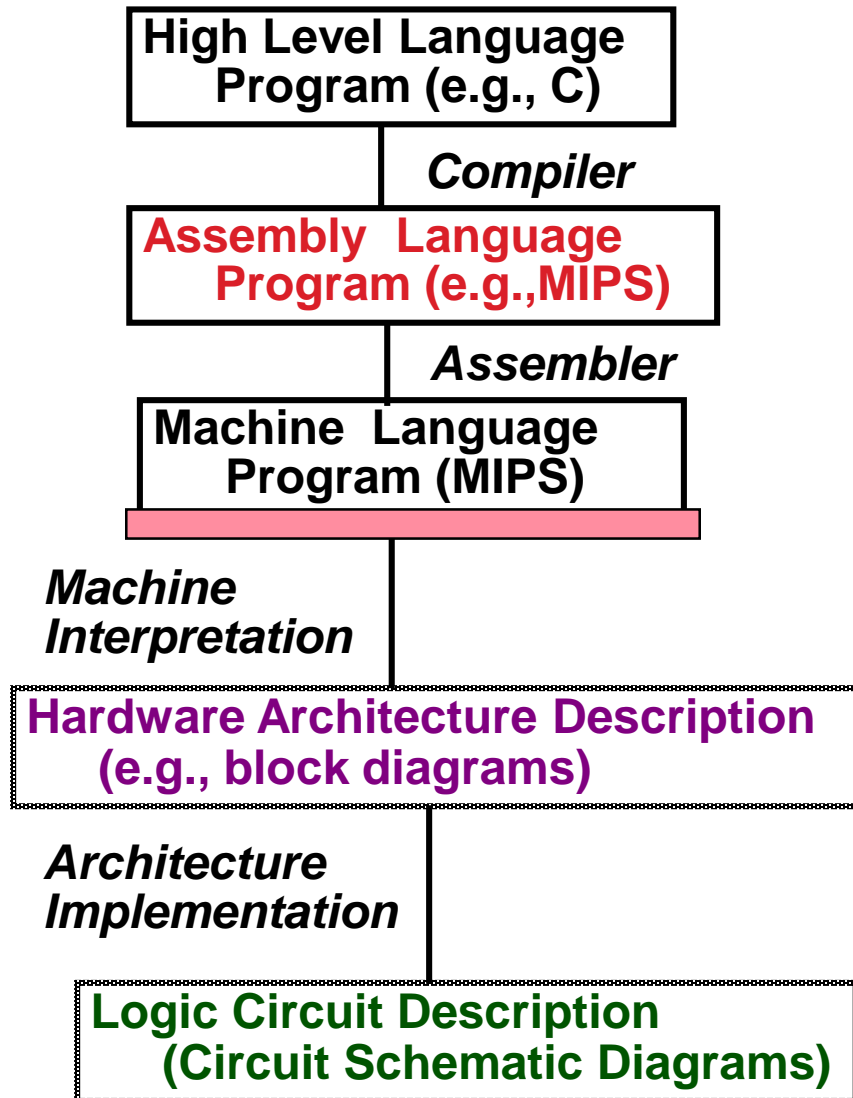

```
temp = v[k];  
v[k] = v[k+1];  
v[k+1] = temp;
```

```
lw    $t0, 0($2)  
lw    $t1, 4($2)  
sw    $t1, 0($2)  
sw    $t0, 4($2)
```

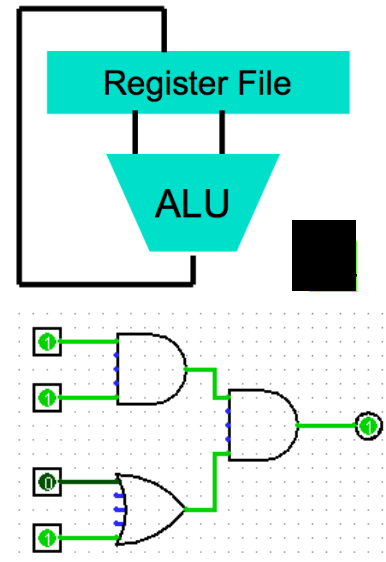
```
0000 1001 1100 0110 1010 1111 0101 1000  
1010 1111 0101 1000 0000 1001 1100 0110  
1100 0110 1010 1111 0101 1000 0000 1001  
0101 1000 0000 1001 1100 0110 1010 1111
```



# Review: Single-cycle Processor

- Five steps to design a processor:

 1. Analyze instruction set → datapath requirements
2. Select set of datapath components & establish clock methodology
3. Assemble datapath meeting the requirements
4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
5. Assemble the control logic
  - Formulate Logic Equations
  - Design Circuits



# Single Cycle Performance

- Assume time for actions are
  - 100ps for register read or write; 200ps for other events
- Clock rate is?

Instr	Instr fetch	Register read	ALU op	Memory access	Register write	Total time
lw	200ps	100 ps	200ps	200ps	100 ps	800ps
sw	200ps	100 ps	200ps	200ps		700ps
R-format	200ps	100 ps	200ps		100 ps	600ps
beq	200ps	100 ps	200ps			500ps

- What can we do to improve clock rate?
- Will this improve performance as well?
  - Want increased clock rate to mean faster programs

# Single Cycle Performance




- Assume time for actions are
  - 100ps for register read or write; 200ps for other events
- Clock rate is?

Instr	Instr fetch	Register read	ALU op	Memory access	Register write	Total time
lw	200ps	100 ps	200ps	200ps	100 ps	800ps
sw	200ps	100 ps	200ps	200ps		700ps
R-format	200ps	100 ps	200ps		100 ps	600ps
beq	200ps	100 ps	200ps			500ps


- What can we do to improve clock rate?
- Will this improve performance as well?
  - Want increased clock rate to mean faster programs
   
# Gotta Do Laundry


- Ann, Brian, Cathy, Dave each have one load of clothes to wash, dry, fold, and put away
  - Washer takes 30 minutes
  - Dryer takes 30 minutes
  - “Folder” takes 30 minutes
  - “Stasher” takes 30 minutes to put clothes into drawers



# Sequential Laundry

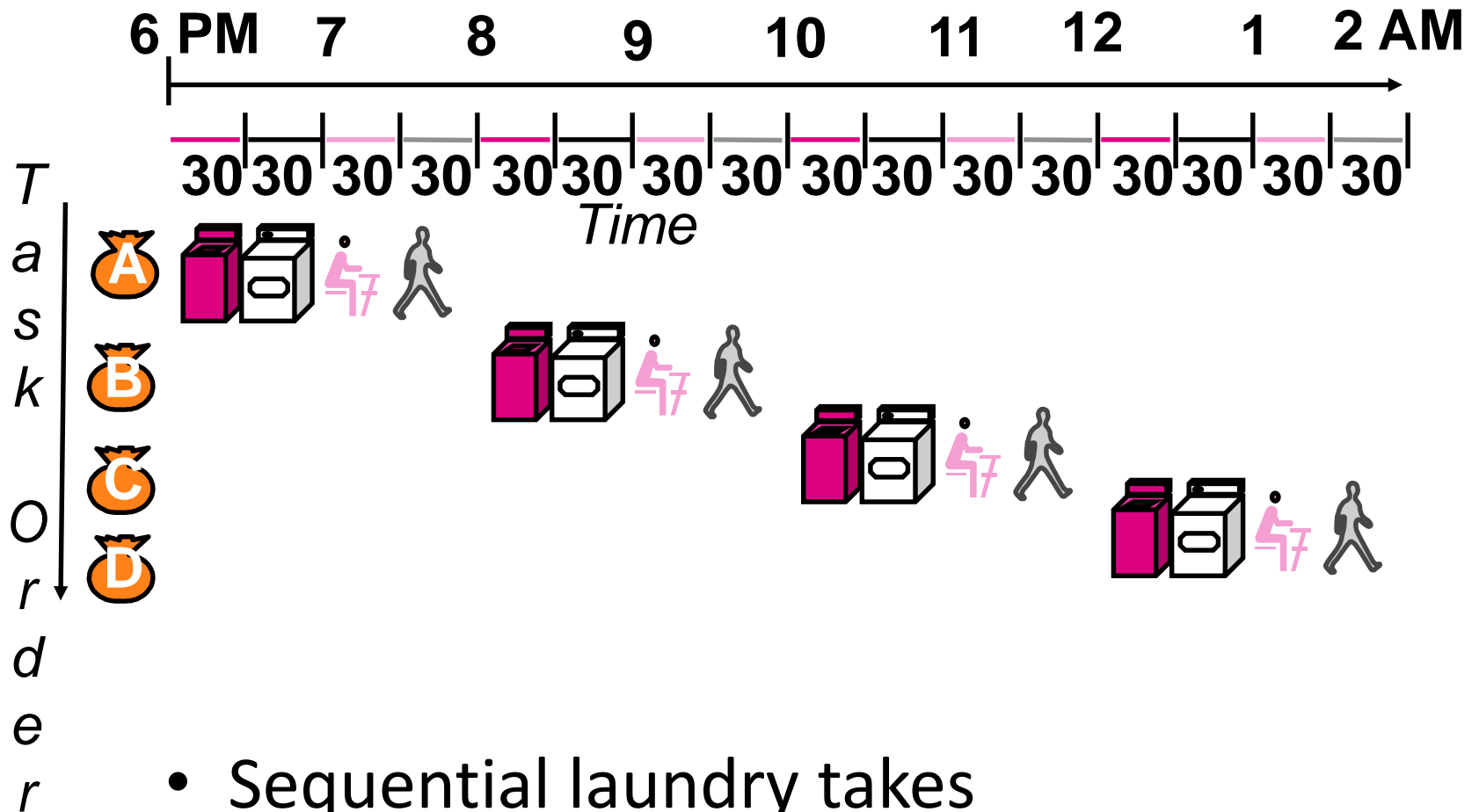


# Pipelined Laundry

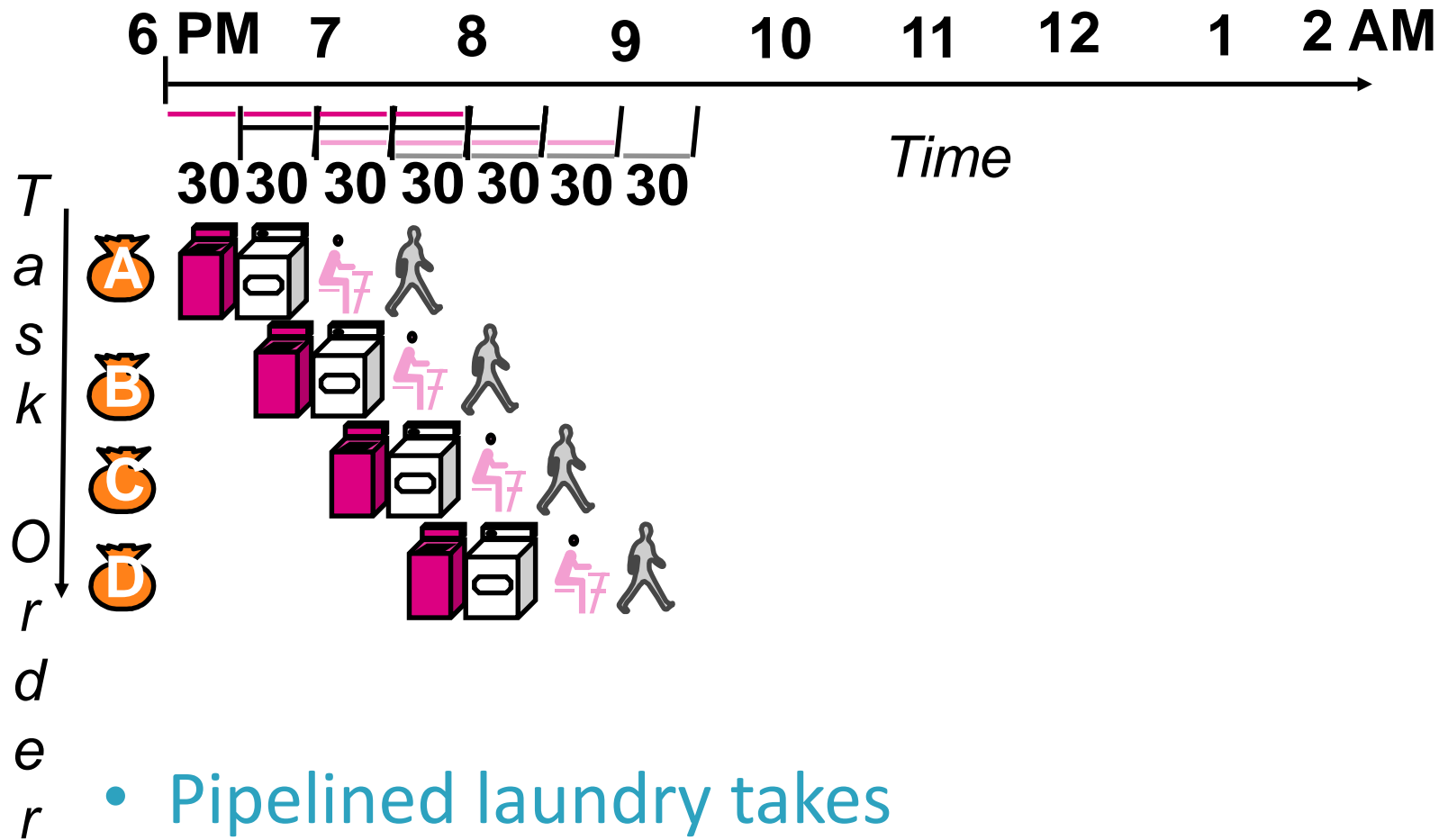




# Pipelining Lessons (1/2)

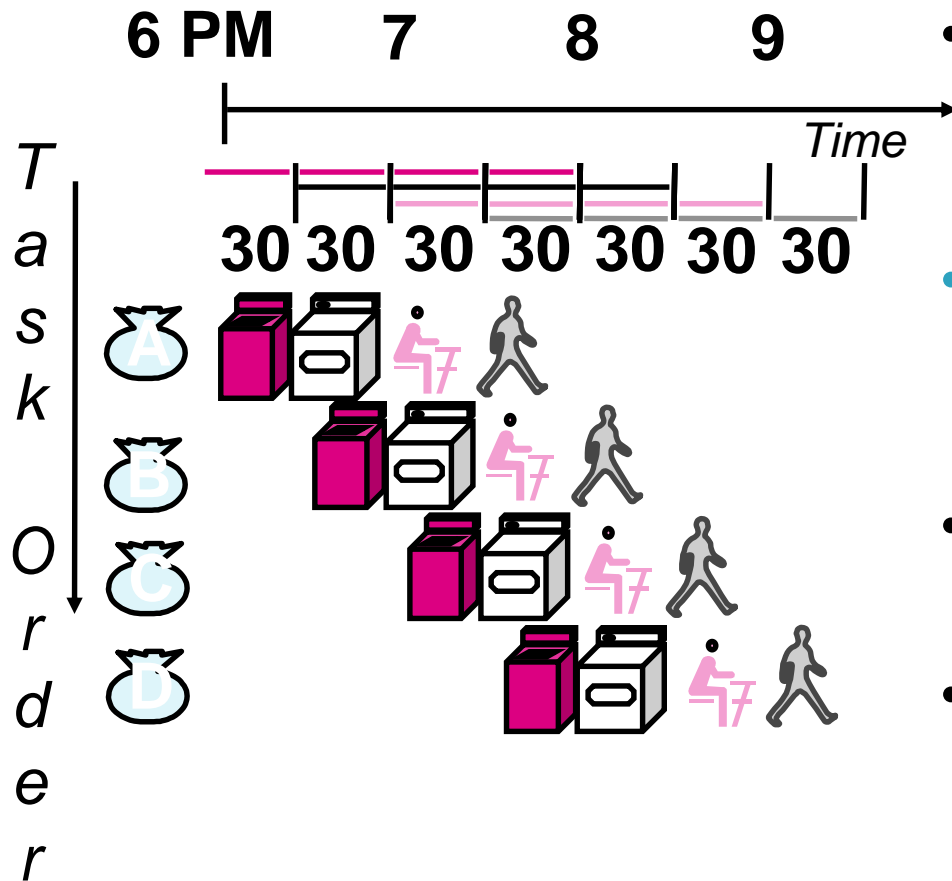

- Pipelining doesn't help latency of single task, it helps throughput of entire workload
- Multiple tasks operating simultaneously using different resources
- Potential speedup = Number pipe stages
- Time to “fill” pipeline and time to “drain” it reduces speedup: 2.3X v. 4X in this example

# Pipelining Lessons (2/2)

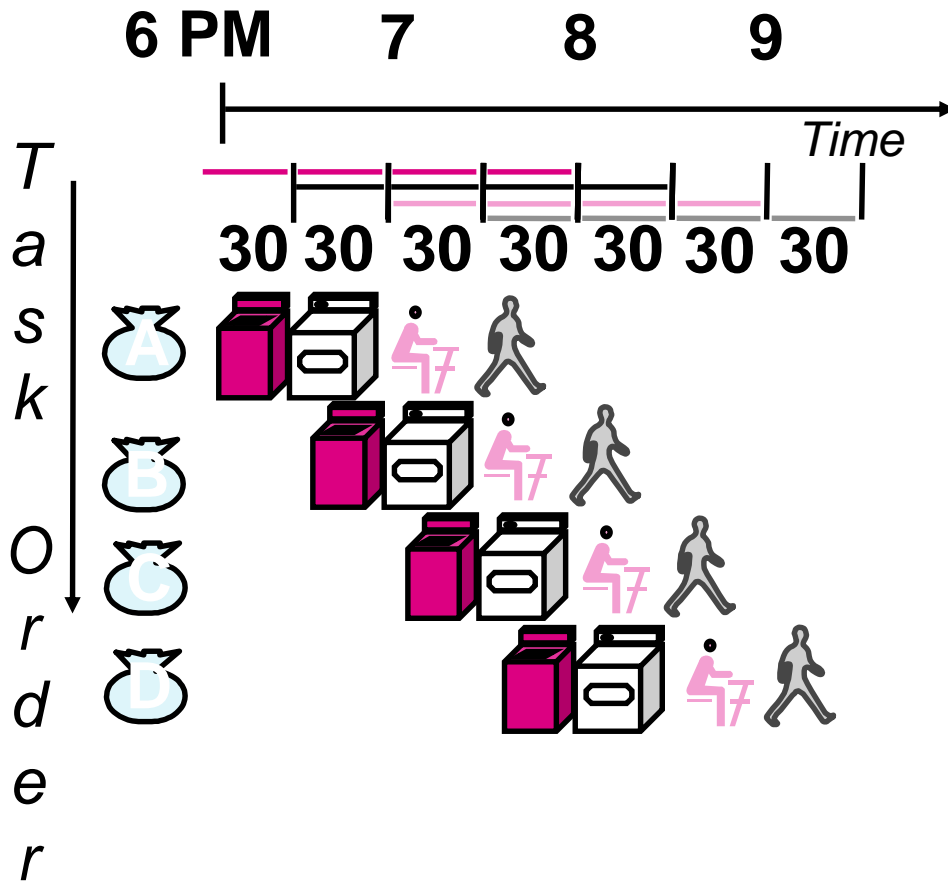


- Suppose new Washer takes 20 minutes, new Stasher takes 20 minutes. How much faster is pipeline?
- Pipeline rate limited by slowest pipeline stage
- Unbalanced lengths of pipe stages reduces speedup


# Steps in Executing MIPS

- 1) IFtch: Instruction Fetch, Increment PC
- 2) Dcd: Instruction Decode, Read Registers
- 3) Exec:
  - Mem-ref: Calculate Address
  - Arith-log: Perform Operation
- 4) Mem:
  - Load: Read Data from Memory
  - Store: Write Data to Memory
- 5) WB: Write Data Back to Register

# Single Cycle Datapath

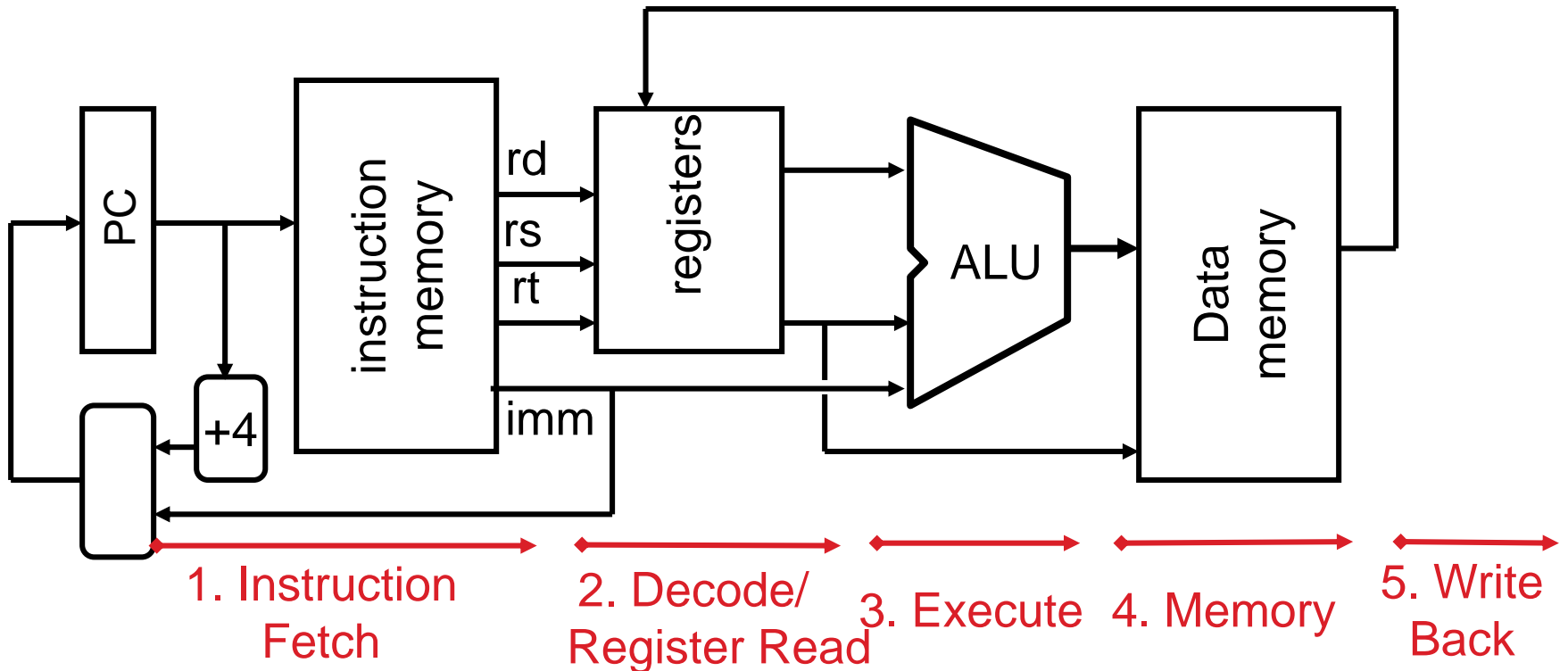


# Pipeline registers

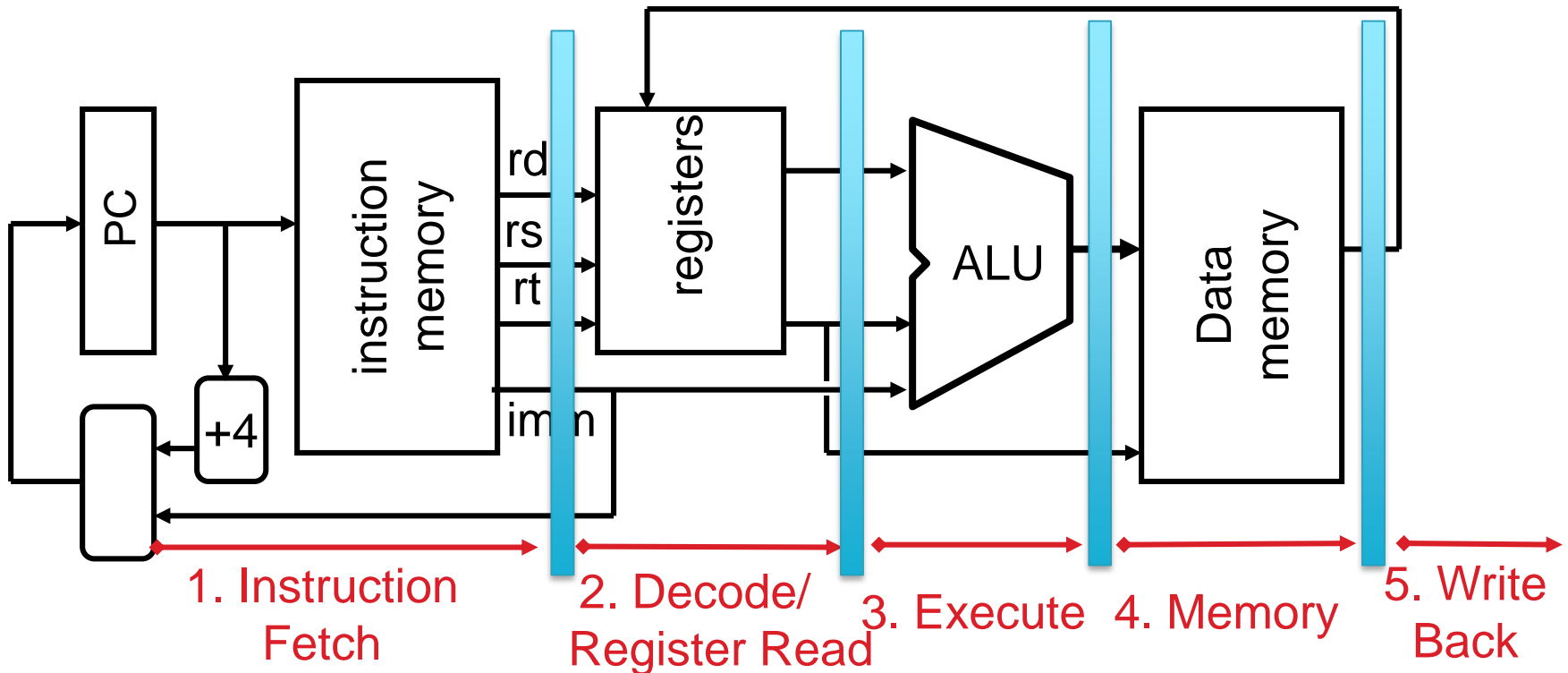


- Need registers between stages
  - To hold information produced in previous cycle


# More Detailed Pipeline

 

# IF for Load, Store, ...

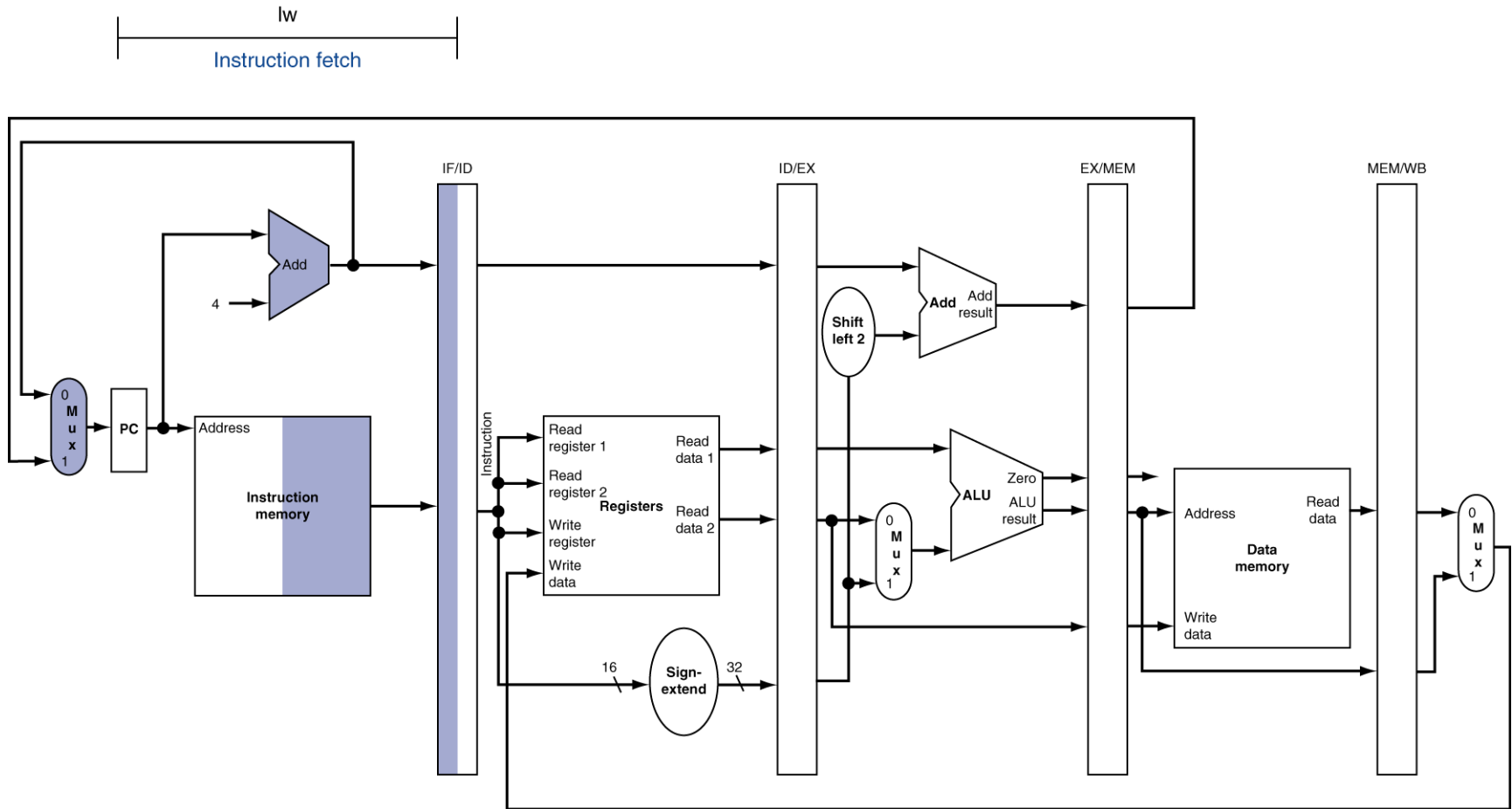


# ID for Load, Store, ...

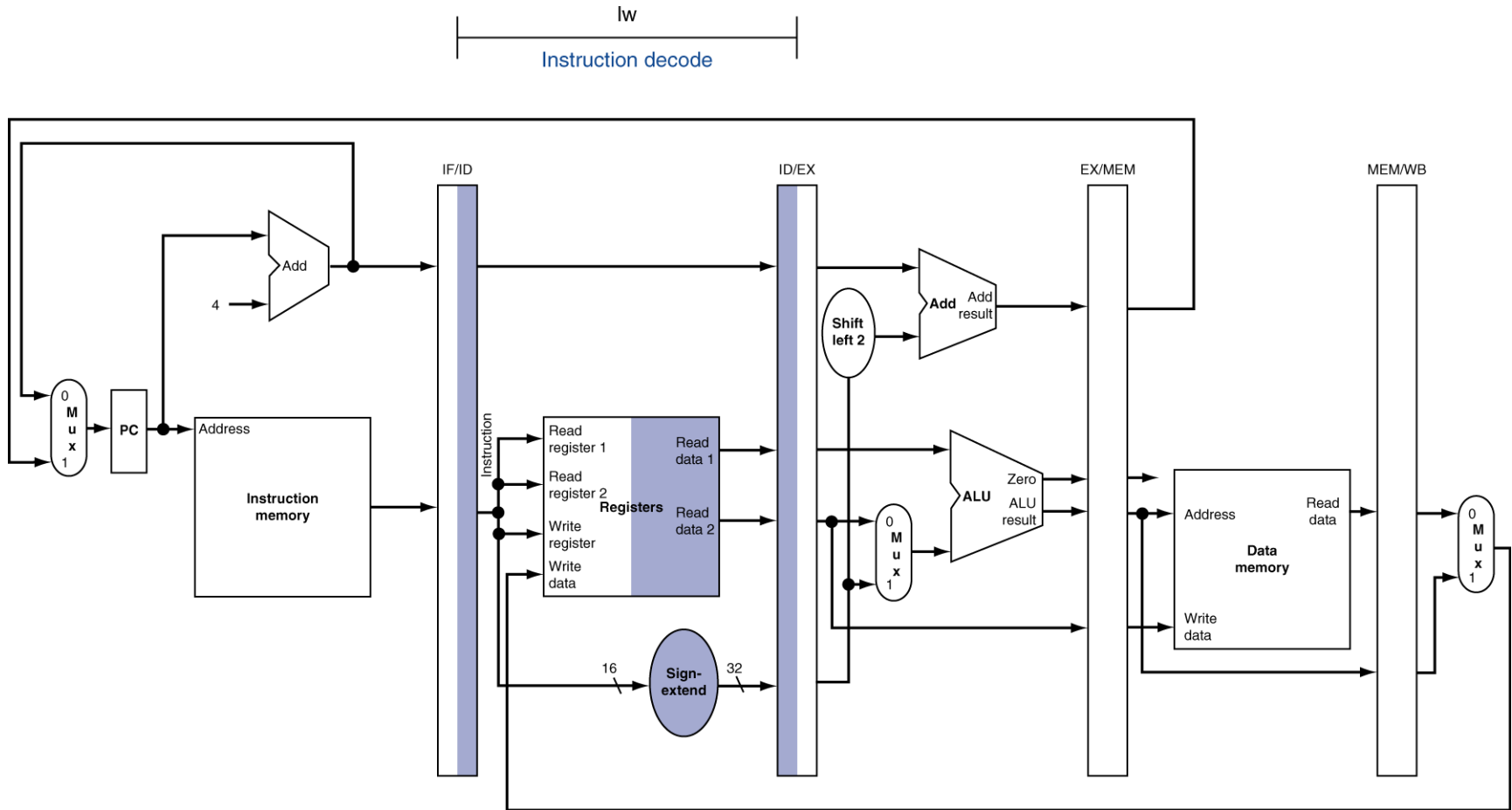





# EX for Load

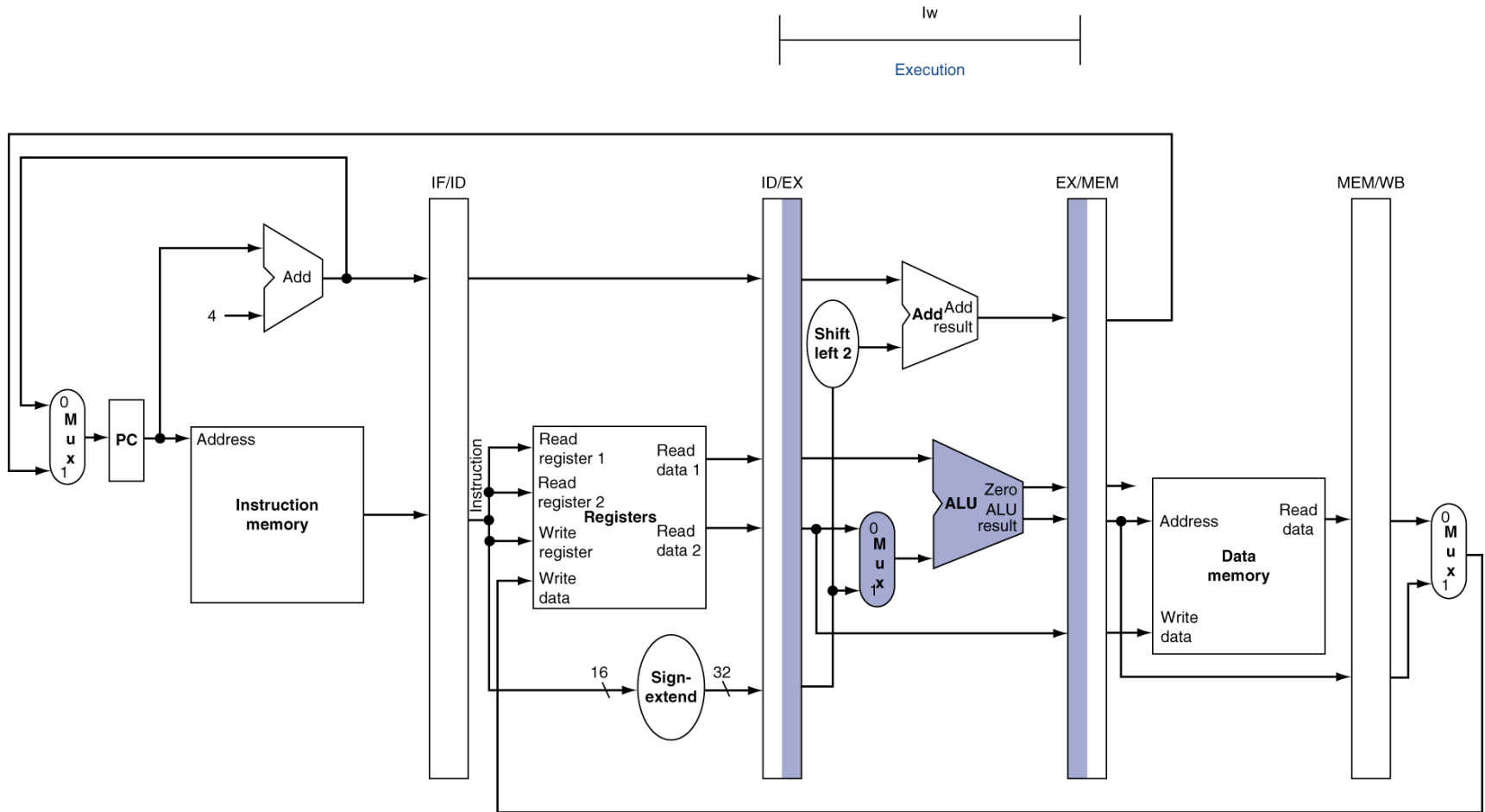


# MEM for Load

 

# WB for Load – Oops!

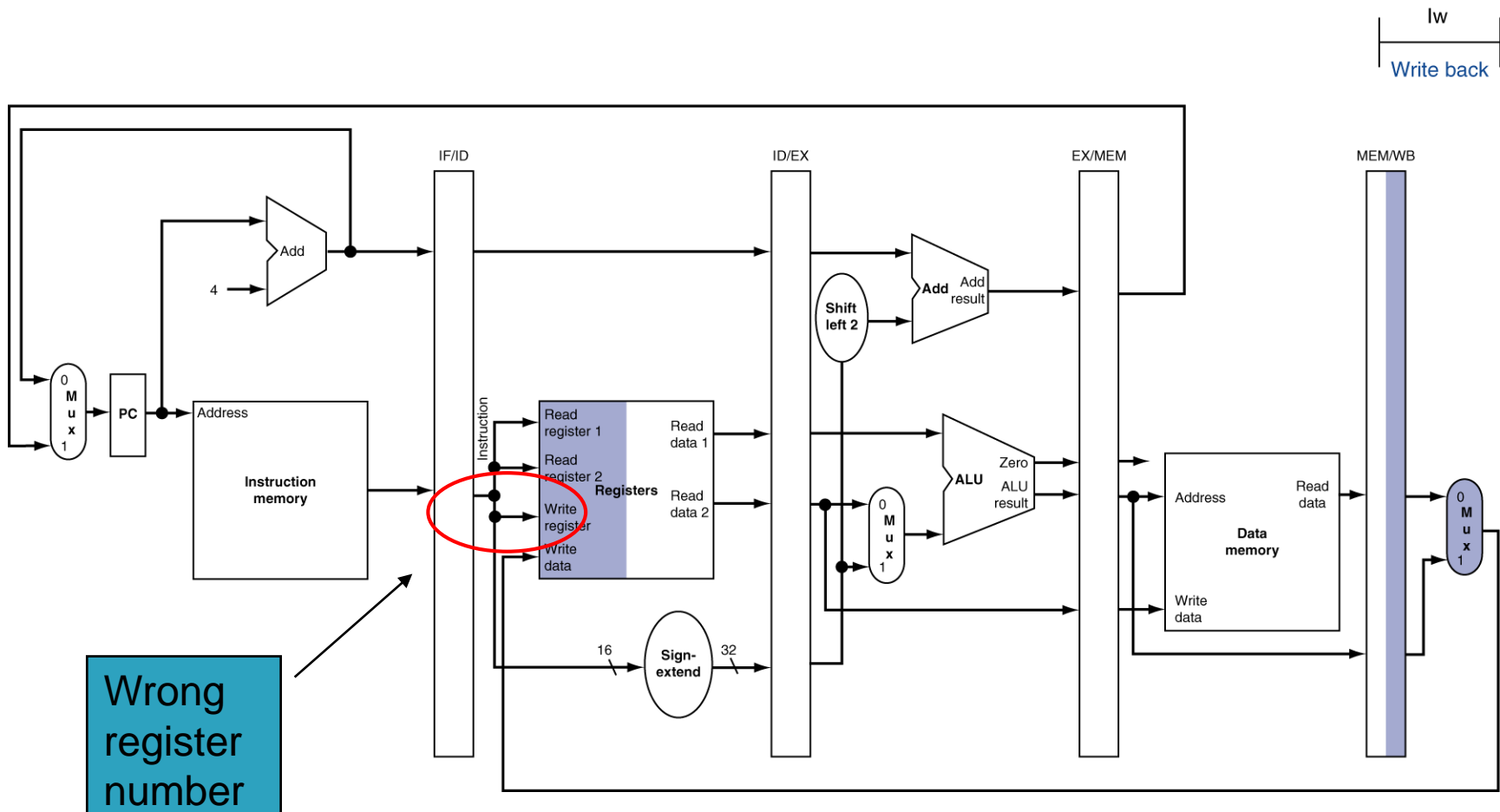

# Corrected Datapath for Load

 

# Peer Instruction

- 1) Thanks to pipelining, I have reduced the time it took me to wash my shirt.
- 2) Longer pipelines are always a win (since less work per stage & a faster clock).
- 3) We can rely on compilers to help us avoid data hazards by reordering instrs.

	123
a:	FFF
b:	FFT
b:	FTF
c:	FTT
c:	TFF
d:	TFT
d:	TTF
e:	TTT

## So, in conclusion

- You now know how to implement the control logic for the single-cycle CPU.
  - (actually, you already knew it!)
- Pipelining improves performance by increasing instruction throughput: exploits ILP
  - Executes multiple instructions in parallel
  - Each instruction has the same latency
- Next: hazards in pipelining:
  - Structure, data, control