

Review: Processor Design 5 steps

Step 1: Analyze instruction set to determine datapath requirements

- Meaning of each instruction is given by register transfers
- Datapath must include storage element for ISA registers
- Datapath must support each register transfer

Step 2: Select set of datapath components & establish clock methodology

Step 3: Assemble datapath components that meet the requirements

Step 4: Analyze implementation of each instruction to determine setting of control points that realizes the register transfer

Step 5: Assemble the control logic

Processor Design: 5 steps

Step 1: Analyze instruction set to determine datapath requirements

- Meaning of each instruction is given by register transfers
- Datapath must include storage element for ISA registers
- Datapath must support each register transfer


Step 2: Select set of datapath components & establish clock methodology

Step 3: Assemble datapath components that meet the requirements



Step 4: Analyze implementation of each instruction to determine setting of control points that realizes the register transfer

Step 5: Assemble the control logic

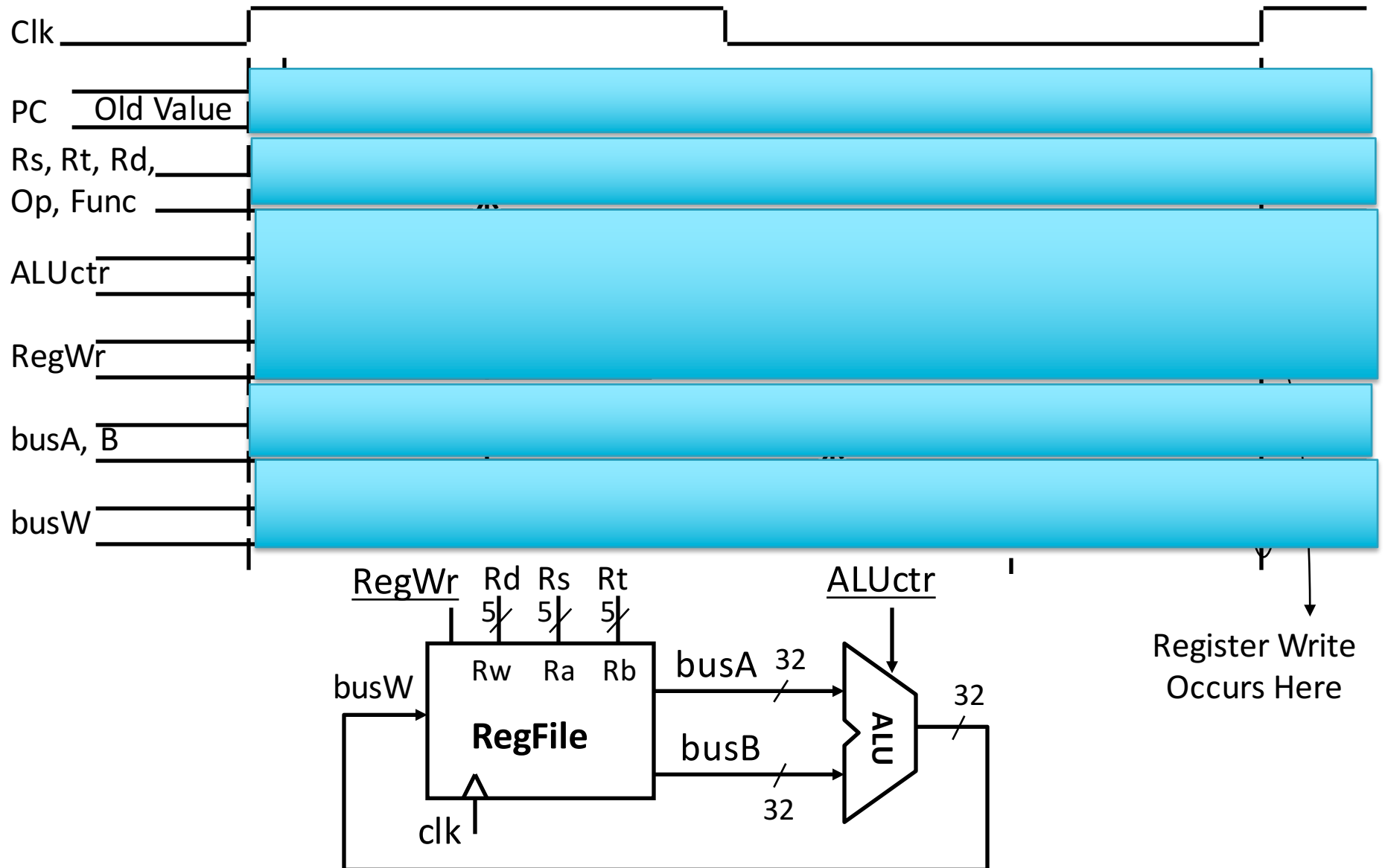Register-Register Timing: One Complete Cycle (Add/Sub)



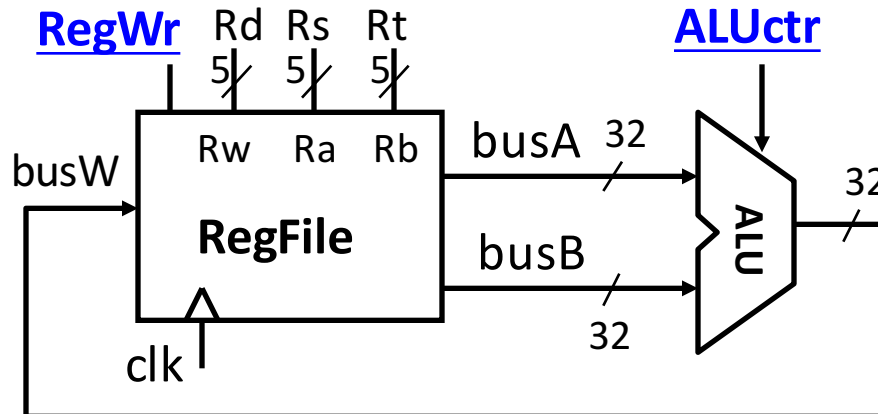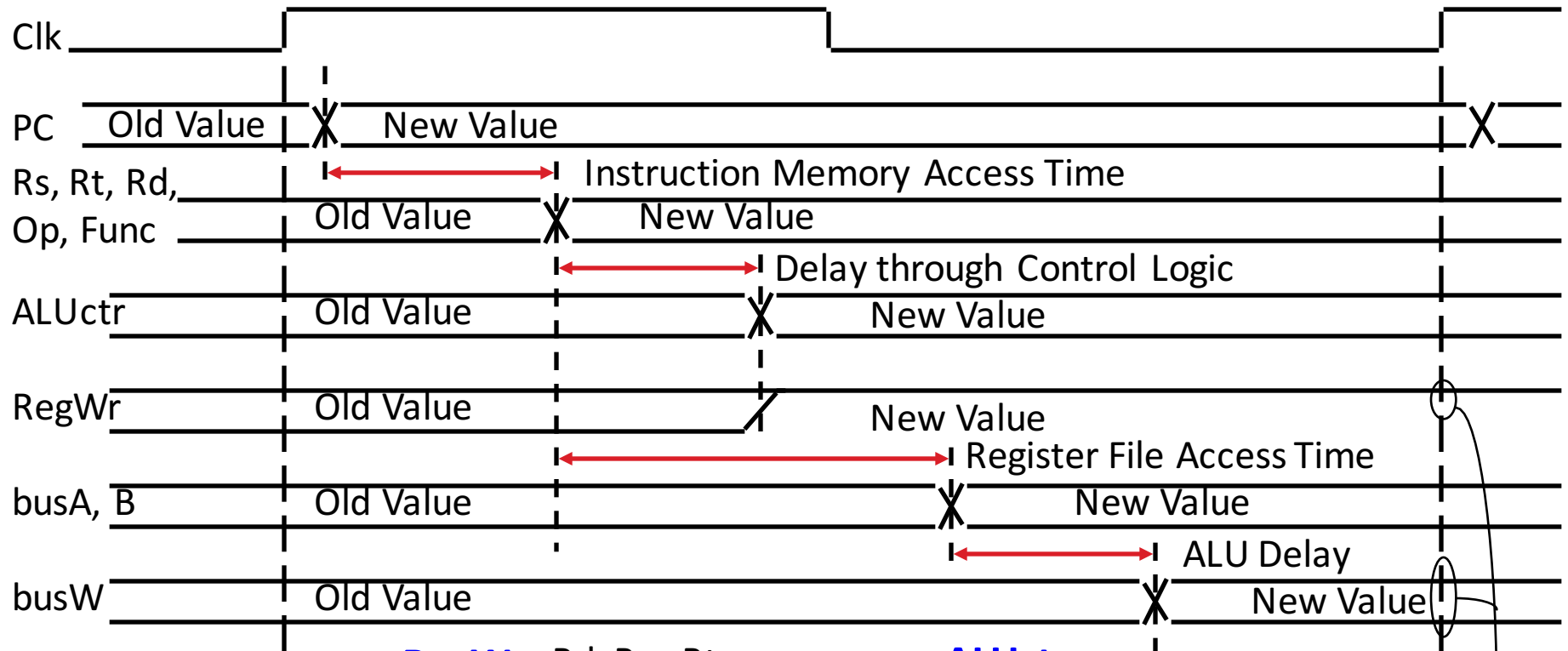
Register-Register Timing: One Complete Cycle



Register Write
Occurs Here


3c: Logical Op (or) with Immediate

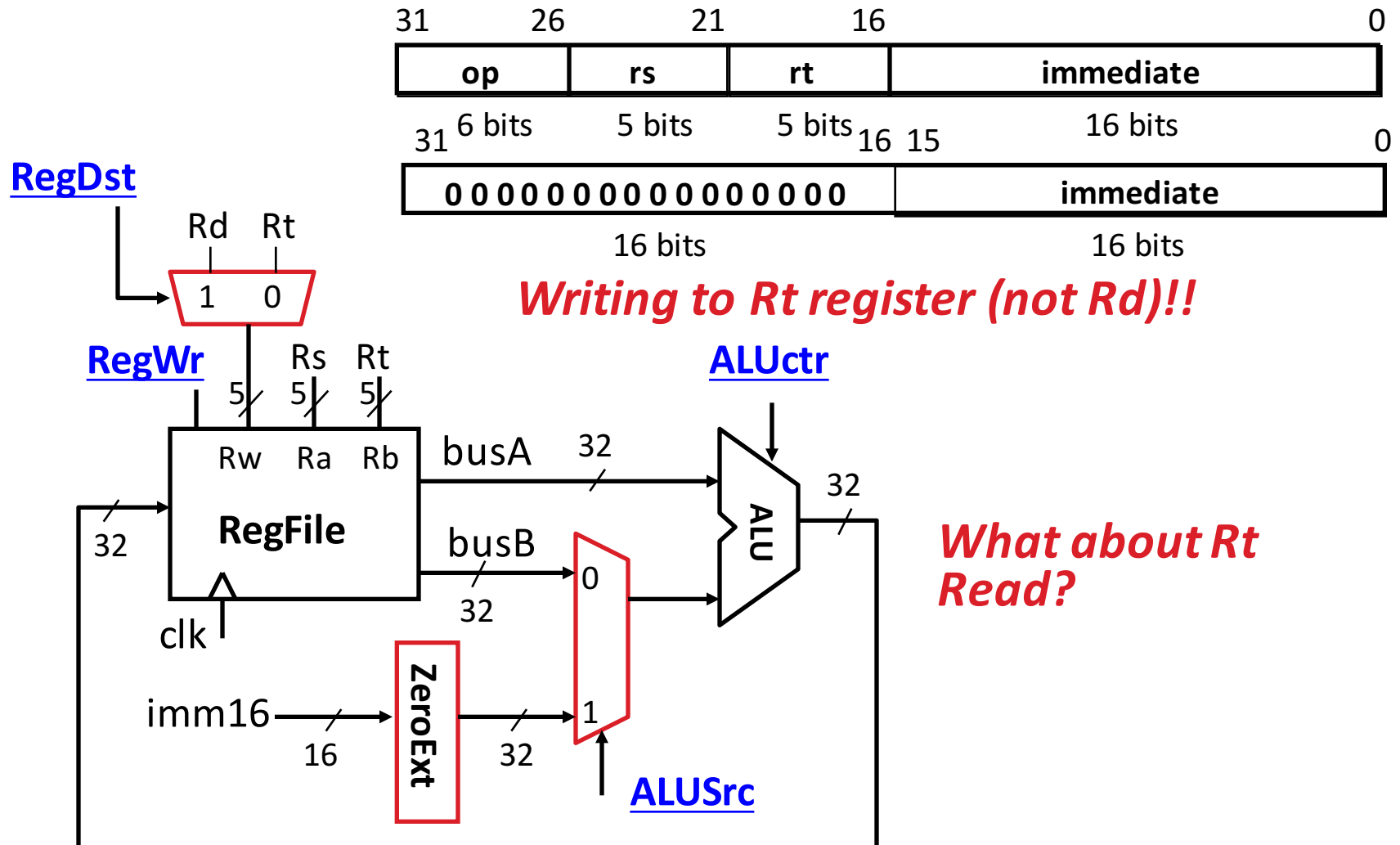- $R[\text{rt}] = R[\text{rs}] \text{ op ZeroExt}[\text{imm16}]$



3d: Load Operations

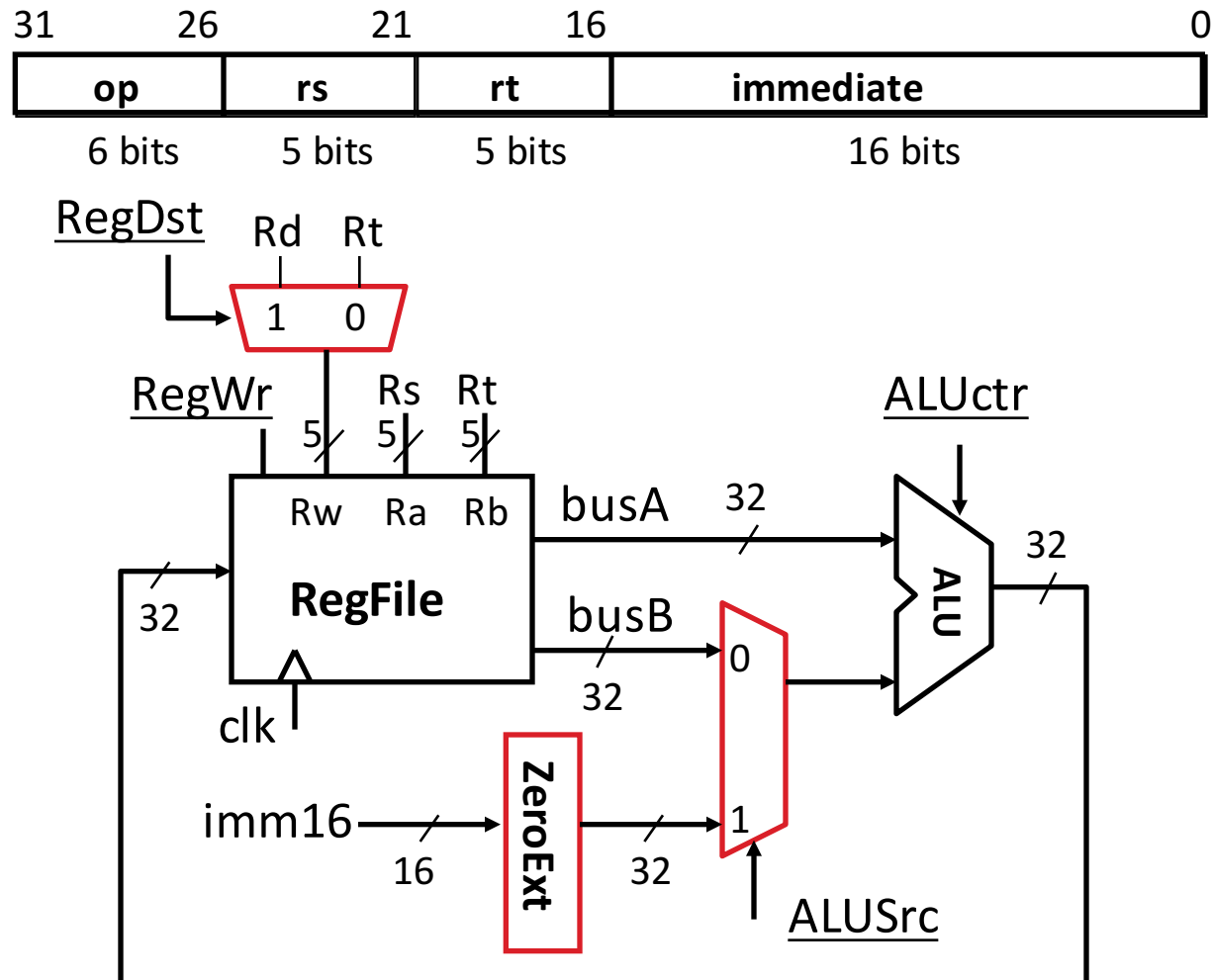
- $R[\text{rt}] = \text{Mem}[R[\text{rs}] + \text{SignExt}[\text{imm16}]]$
Example: `lw rt, rs, imm16`



3d: Load Operations

- $R[\text{rt}] = \text{Mem}[R[\text{rs}] + \text{SignExt}[\text{imm16}]]$



Example: `lw rt, rs, imm16`

 

3e: Store Operations

- Mem[R[rs] + SignExt[imm16]] = R[rt]



Ex.: sw rt, rs, imm16

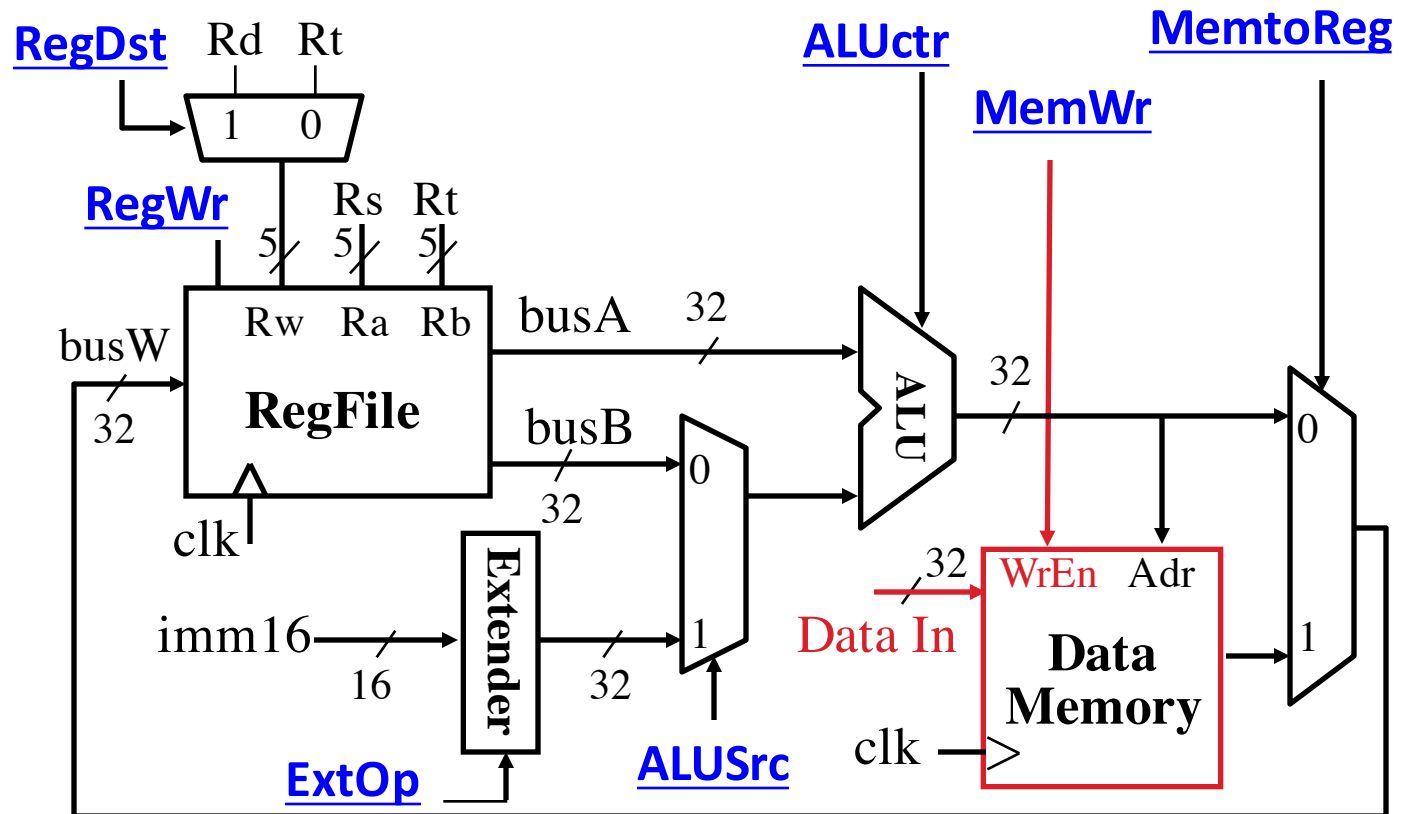 


3e: Store Operations

- Mem[R[rs] + SignExt[imm16]] = R[rt]

Ex.: sw rt, rs, imm16

  

3f: The Branch Instruction

 

`beq rs, rt, imm16`


- `mem[PC]` Fetch the instruction from memory
- `Equal = R[rs] == R[rt]` Calculate branch condition
- if (Equal) Calculate the next instruction's address
 - $PC = PC + 4 + (\text{SignExt}(\text{imm16}) \times 4)$

else

- $PC = PC + 4$


Datapath for Branch Operations

beq rs, rt, imm16

 


Datapath generates condition (Equal)

Inst Address

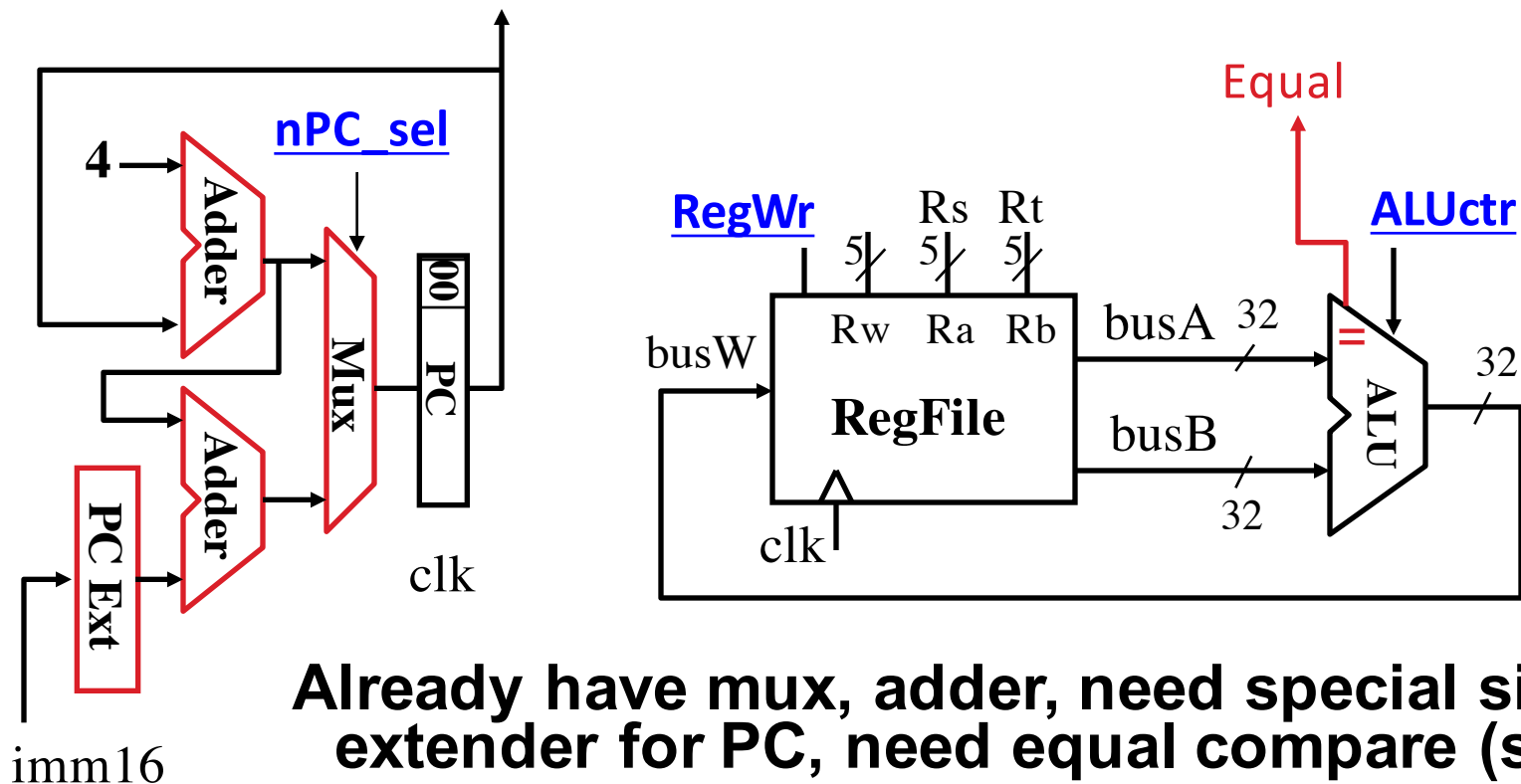


Already have mux, adder, need special sign extender for PC, need equal compare (sub?)

Instruction Fetch Unit including Branch

 

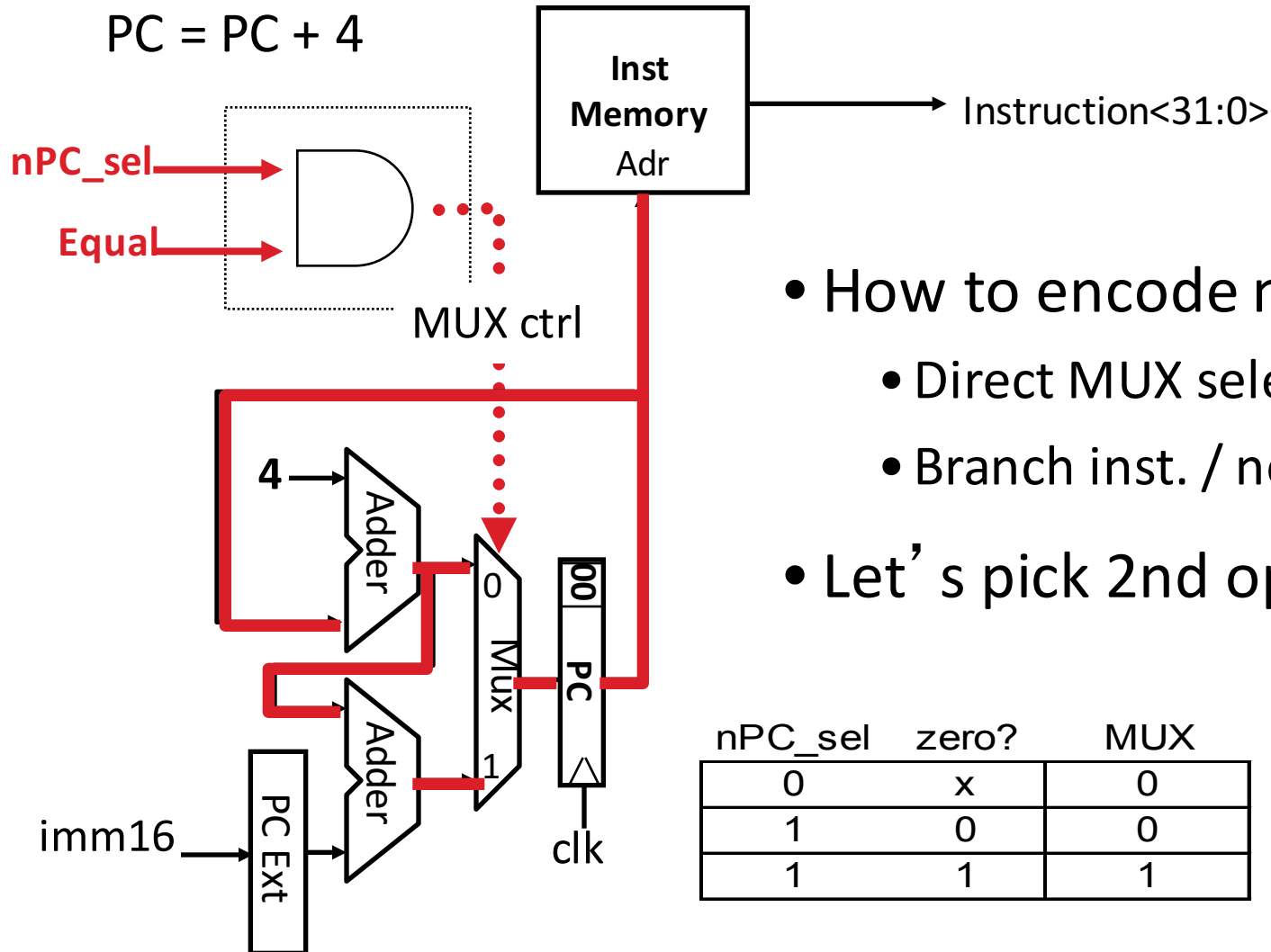- if (Zero == 1) then $PC = PC + 4 + \text{SignExt}[\text{imm16}] * 4$; else $PC = PC + 4$




- How to encode nPC_sel?
 - Direct MUX select?
 - Branch inst. / not branch inst.
- Let's pick 2nd option

nPC_sel	zero?	MUX
0	x	0
1	0	0
1	1	1

Q: What logic gate?




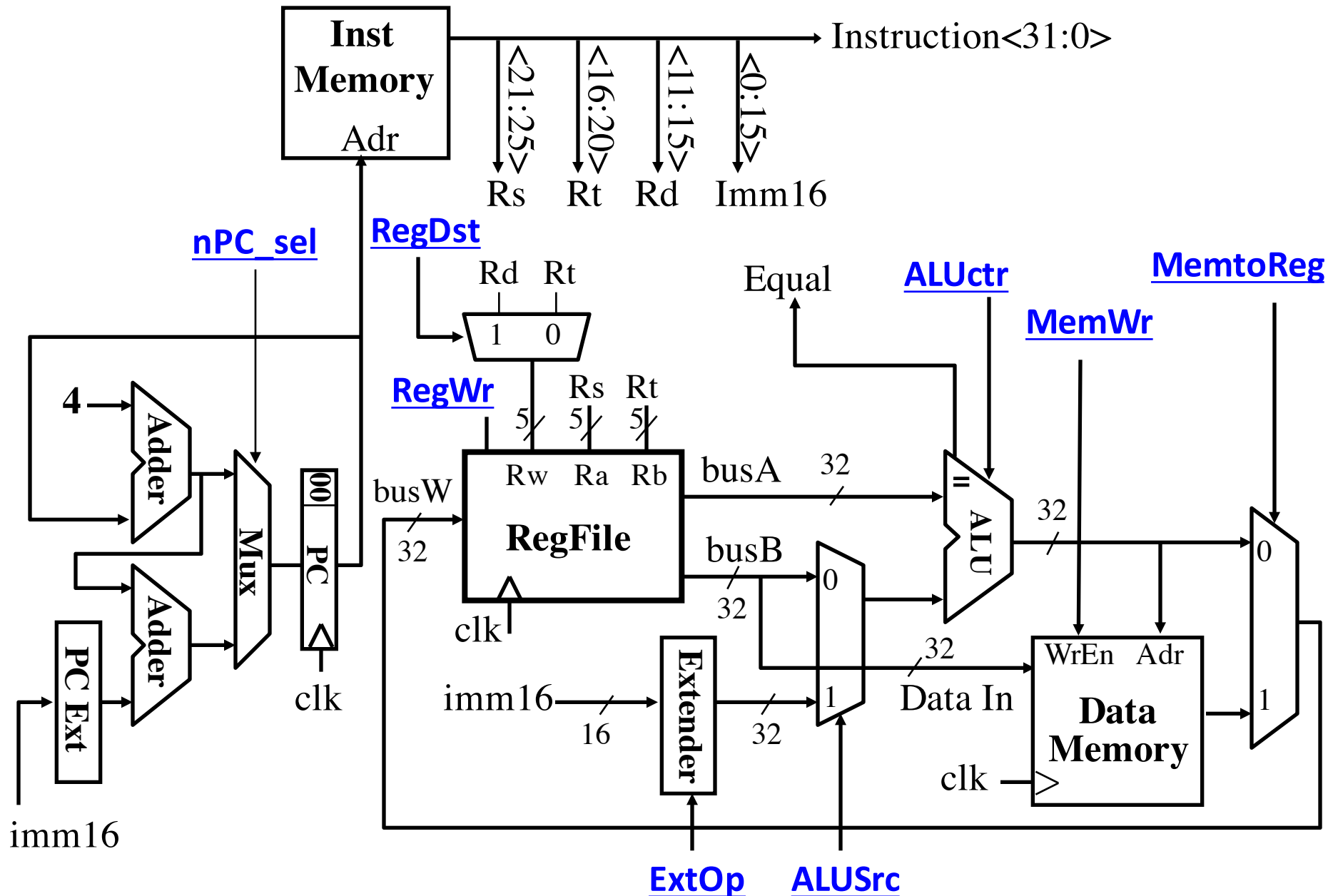Putting it All Together: A Single Cycle Datapath




Datapath Control Signals

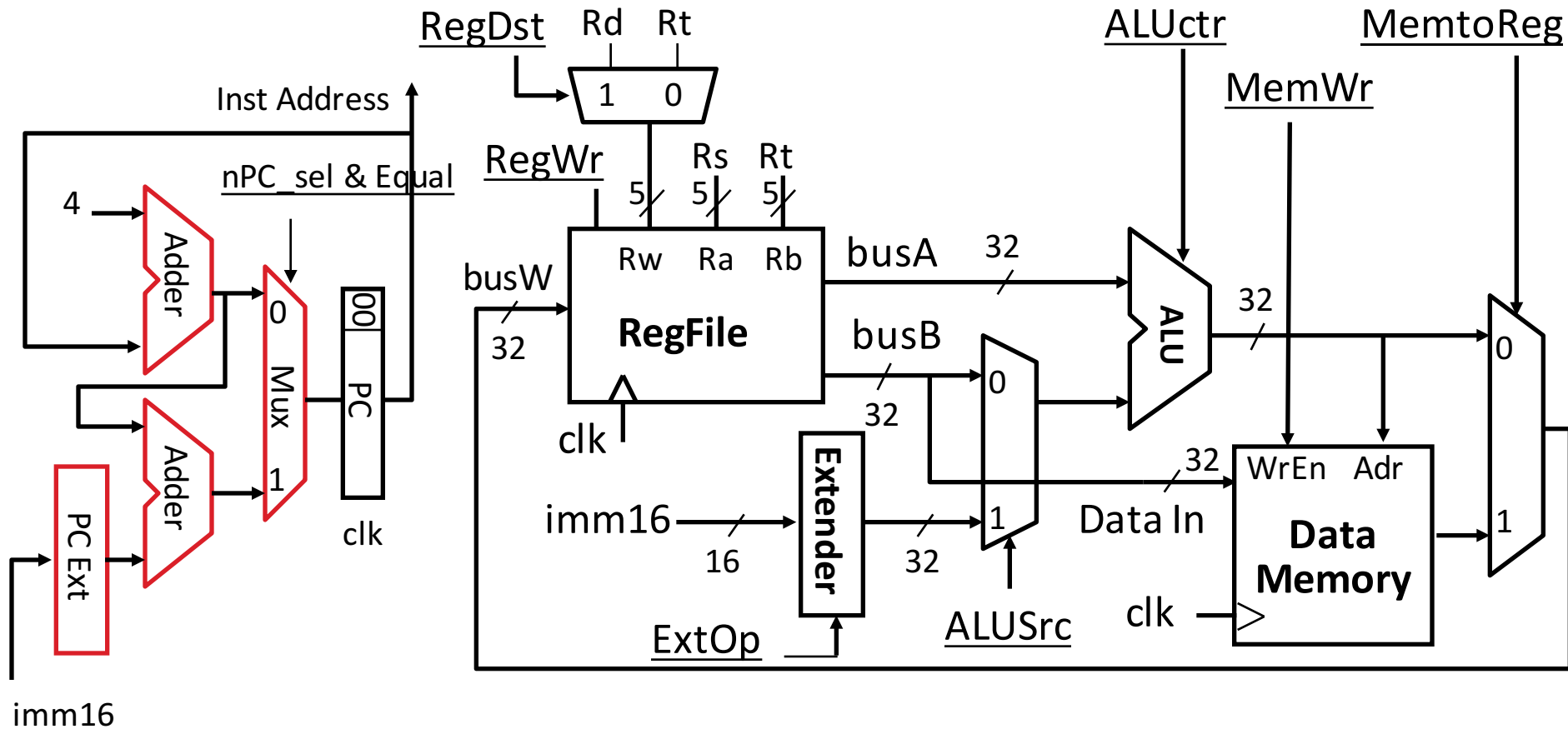
- ExtOp: “zero”, “sign”
- ALUsrc: 0 \Rightarrow regB;
1 \Rightarrow immedi
- ALUctr: “ADD”, “SUB”, “OR”
- MemWr: 1 \Rightarrow write memory
- MemtoReg: 0 \Rightarrow ALU; 1 \Rightarrow Mem
- RegDst: 0 \Rightarrow “rt”; 1 \Rightarrow “rd”
- RegWr: 1 \Rightarrow write register



Given Datapath: RTL \rightarrow Control

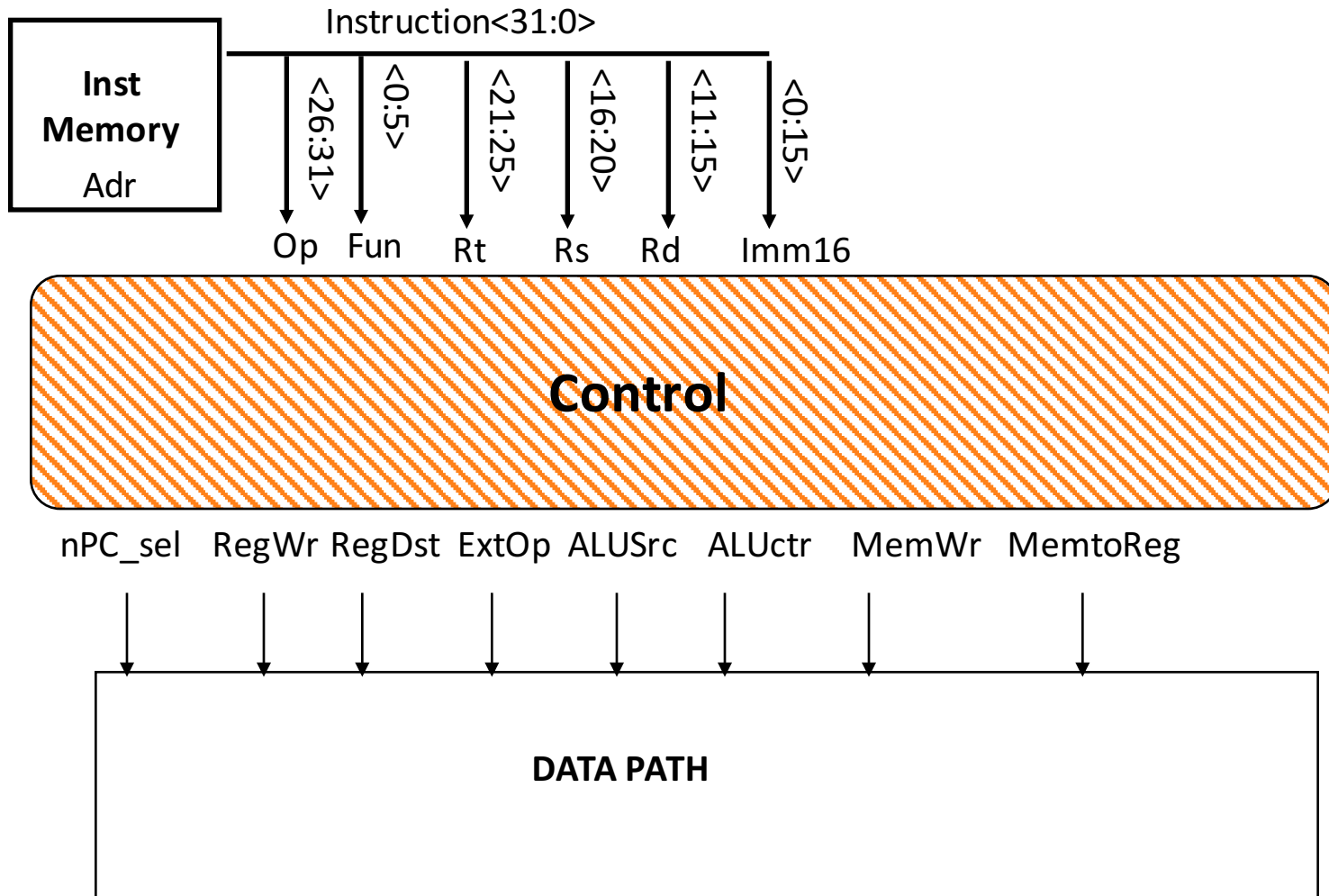

RTL: The Add Instruction

 


add rd, rs, rt

- MEM[PC] Fetch the instruction from memory
- $R[rd] = R[rs] + R[rt]$ The actual operation
- $PC = PC + 4$ Calculate the next instruction's address


Instruction Fetch Unit at the Beginning of Add

- Fetch the instruction from Instruction memory: $\text{Instruction} = \text{MEM}[\text{PC}]$


– same for all instructions

 

Single Cycle Datapath during Add

 


$$R[rd] = R[rs] + R[rt]$$

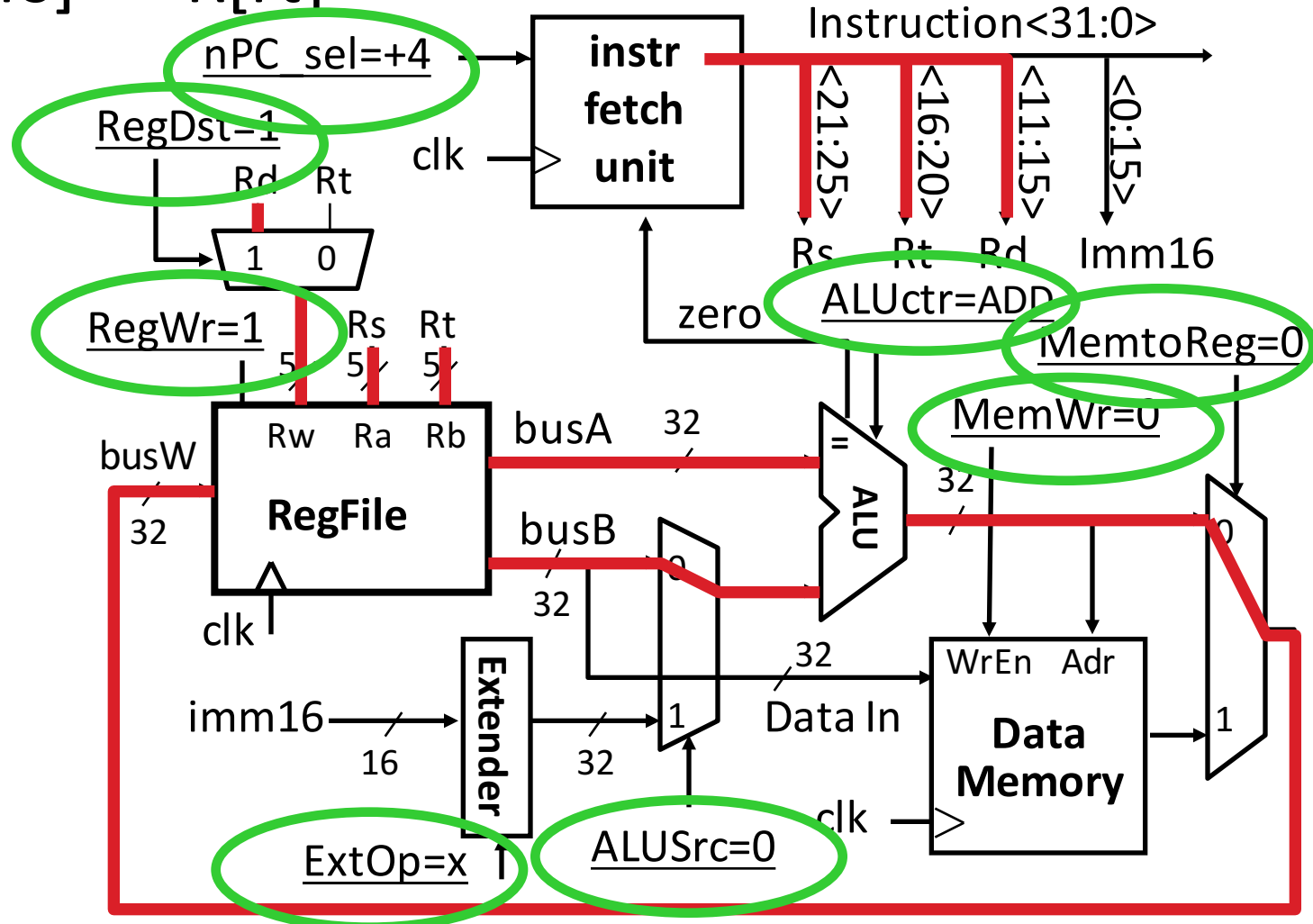


Instruction Fetch Unit at End of Add

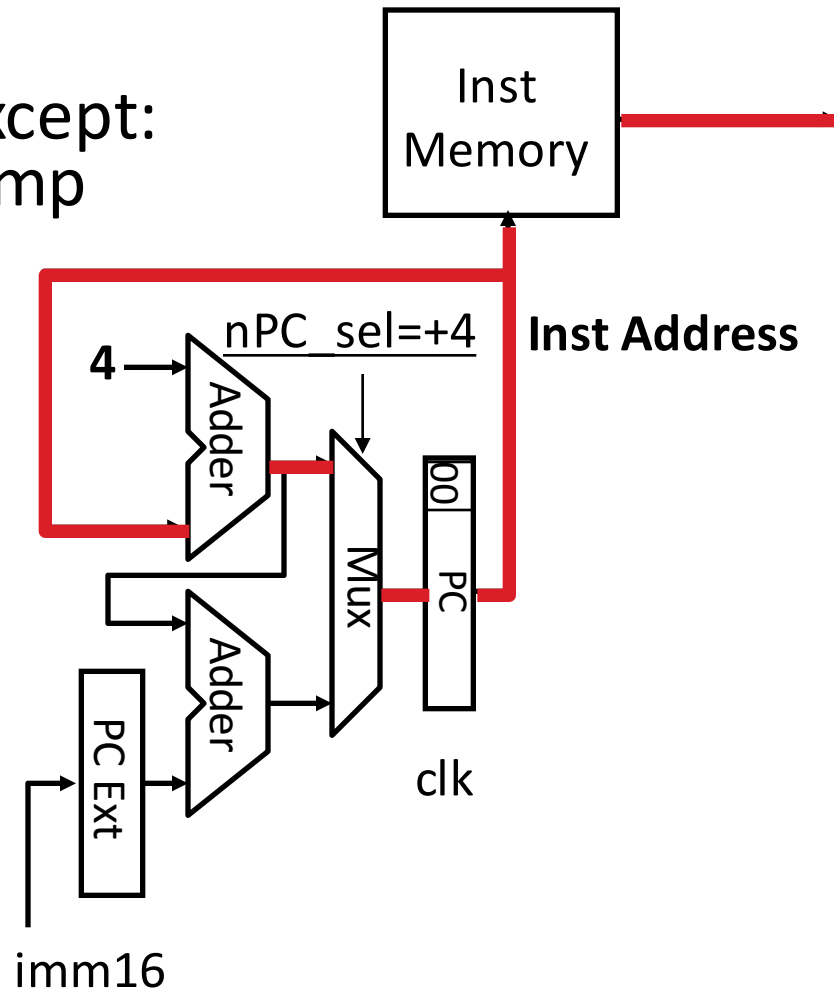- $PC = PC + 4$
 - Same for all instructions except: Branch and Jump



P&H Figure 4.17

 

Summary of the Control Signals (1/2)

inst Register Transfer

add $R[rd] \leftarrow R[rs] + R[rt]; PC \leftarrow PC + 4$

ALUsrc=RegB, ALUctr="ADD", RegDst=rd, RegWr, nPC_sel="+4"

sub $R[rd] \leftarrow R[rs] - R[rt]; PC \leftarrow PC + 4$

ALUsrc=RegB, ALUctr="SUB", RegDst=rd, RegWr, nPC_sel="+4"

ori $R[rt] \leftarrow R[rs] + \text{zero_ext}(\text{Imm16}); PC \leftarrow PC + 4$

ALUsrc=Im, Extop="Z", ALUctr="OR", RegDst=rt, RegWr, nPC_sel="+4"

lw $R[rt] \leftarrow \text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})]; PC \leftarrow PC + 4$

ALUsrc=Im, Extop="sn", ALUctr="ADD", MemtoReg, RegDst=rt, RegWr,
nPC_sel = "+4"

sw $\text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})] \leftarrow R[rs]; PC \leftarrow PC + 4$

ALUsrc=Im, Extop="sn", ALUctr = "ADD", MemWr, nPC_sel = "+4"

beq if ($R[rs] == R[rt]$) then $PC \leftarrow PC + \text{sign_ext}(\text{Imm16})$ || 00
 else $PC \leftarrow PC + 4$

nPC_sel = "br", ALUctr = "SUB"

Summary of the Control Signals (2/2)

See Appendix A

func

op

	10 0000	10 0010	We Don't Care :-)				
	00 0000	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	add	sub	ori	lw	sw	beq	jump
RegDst	1	1	0	0	x	x	x
ALUSrc	0	0	1	1	1	0	x
MemtoReg	0	0	0	1	x	x	x
RegWrite	1	1	1	1	0	0	0
MemWrite	0	0	0	0	1	0	0
nPCsel	0	0	0	0	0	1	?
Jump	0	0	0	0	0	0	1
ExtOp	x	x	0	1	1	x	x
ALUctr<2:0>	Add	Subtract	Or	Add	Add	Subtract	x

	31	26	21	16	11	6	0						
R-type	op		rs		rt		rd		shamt		funct		add, sub
I-type	op		rs		rt		immediate						ori, lw, sw, beq
J-type	op		target address										jump

Boolean Expressions for Controller

```
RegDst      = add + sub
ALUSrc      = ori + lw + sw
MemtoReg    = lw
RegWrite    = add + sub + ori + lw
MemWrite    = sw
nPCsel      = beq
Jump        = jump
ExtOp       = lw + sw
ALUctr[0]   = sub + beq    (assume ALUctr is 00 ADD, 01 SUB, 10 OR)
ALUctr[1]   = or
```


Where:

```
rtype = ~op5 • ~op4 • ~op3 • ~op2 • ~op1 • ~op0,
ori    = ~op5 • ~op4 • op3 • op2 • ~op1 • op0
lw     = op5 • ~op4 • ~op3 • ~op2 • op1 • op0
sw     = op5 • ~op4 • op3 • ~op2 • op1 • op0
beq    = ~op5 • ~op4 • ~op3 • op2 • ~op1 • ~op0
jump   = ~op5 • ~op4 • ~op3 • ~op2 • op1 • ~op0
```

```
add = rtype • func5 • ~func4 • ~func3 • ~func2 • ~func1 • ~func0
sub = rtype • func5 • ~func4 • ~func3 • ~func2 • func1 • ~func0
```

How do we
implement this in
gates?

Controller Implementation

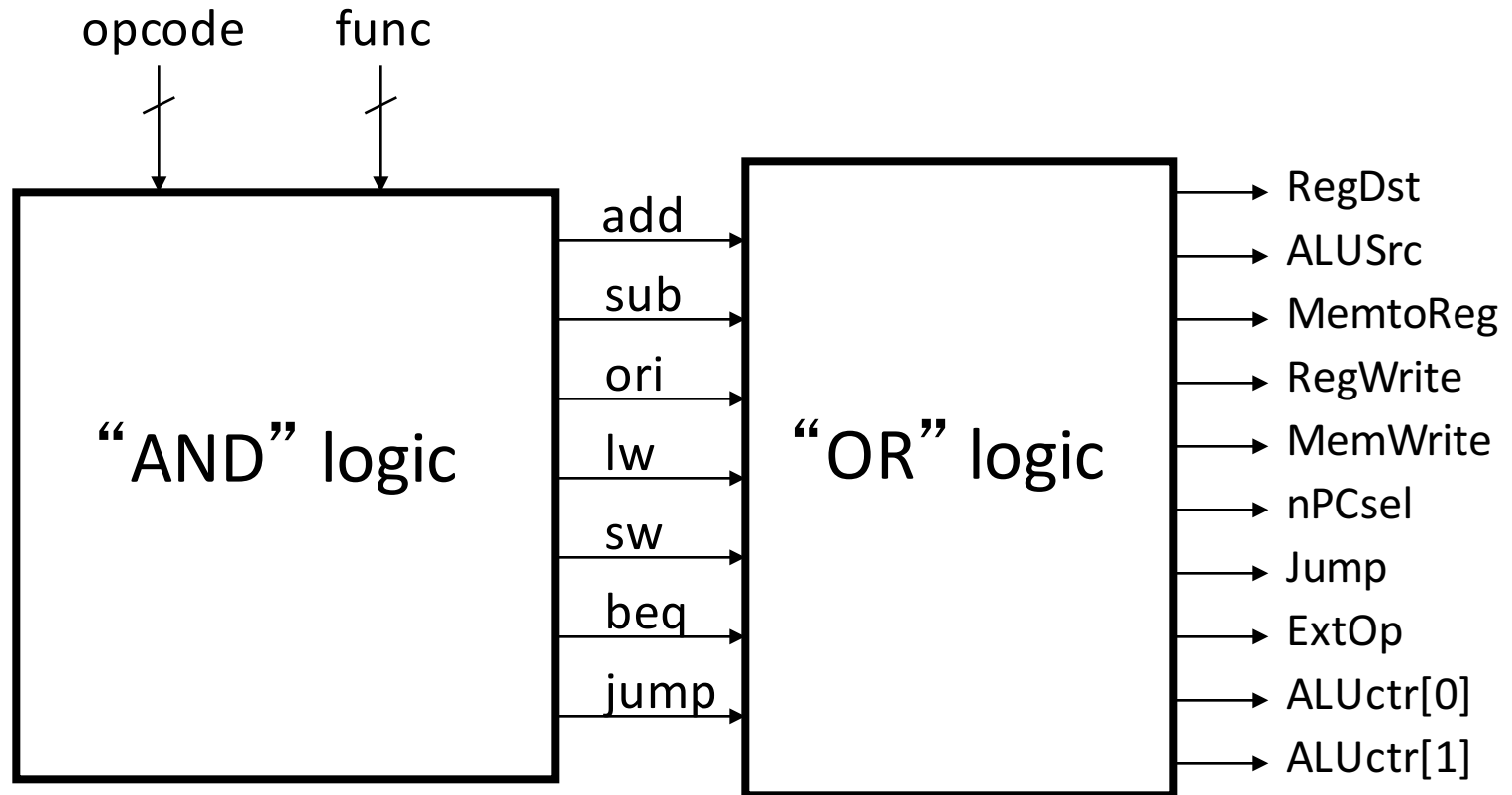

Peer Instruction

- 1) We **should use the main ALU** to compute $PC = PC + 4$ in order to save some gates
- 2) The **ALU is inactive** for memory reads (loads) or writes (stores).

	12
a)	FF
b)	FT
c)	TF
d)	TT
e)	Help!

Clicker Survey for CS Retreat


If we add more faculty, what should we do for upper-division courses?

- a) We should have more sections of the same courses, so lecture is smaller
- b) We should have more semester-long courses
- c) We should have more half-semester-long courses

Summary: Single-cycle Processor

- Five steps to design a processor:

 1. Analyze instruction set → datapath requirements
2. Select set of datapath components & establish clock methodology
3. Assemble datapath meeting the requirements
4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
5. Assemble the control logic
 - Formulate Logic Equations
 - Design Circuits




Bonus Slides

- How to implement Jump

Single Cycle Datapath during Jump



 
- New PC = { PC[31..28], target address, 00 }



Single Cycle Datapath during Jump



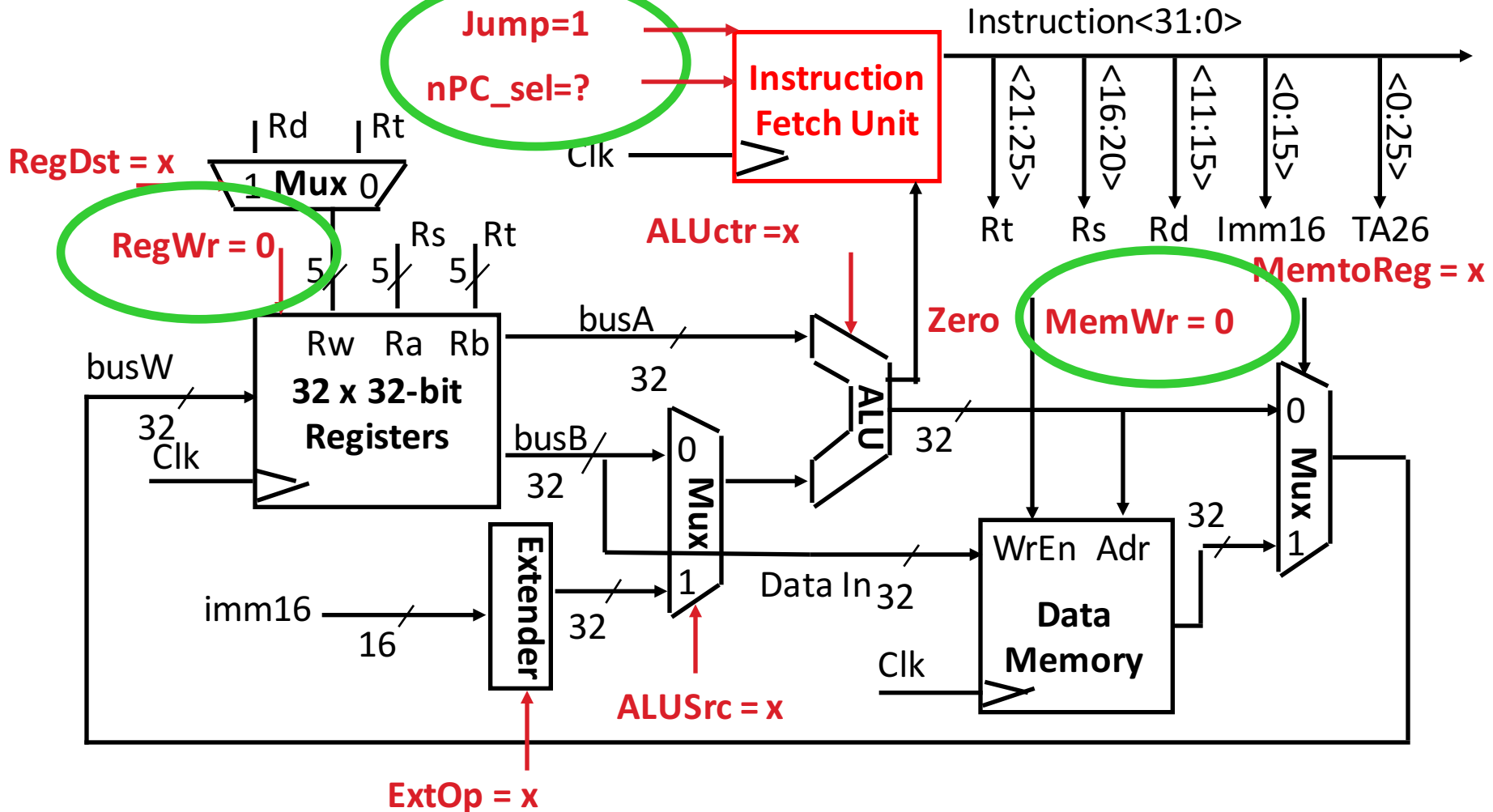
- New PC = { PC[31..28], target address, 00 }



Instruction Fetch Unit at the End of Jump



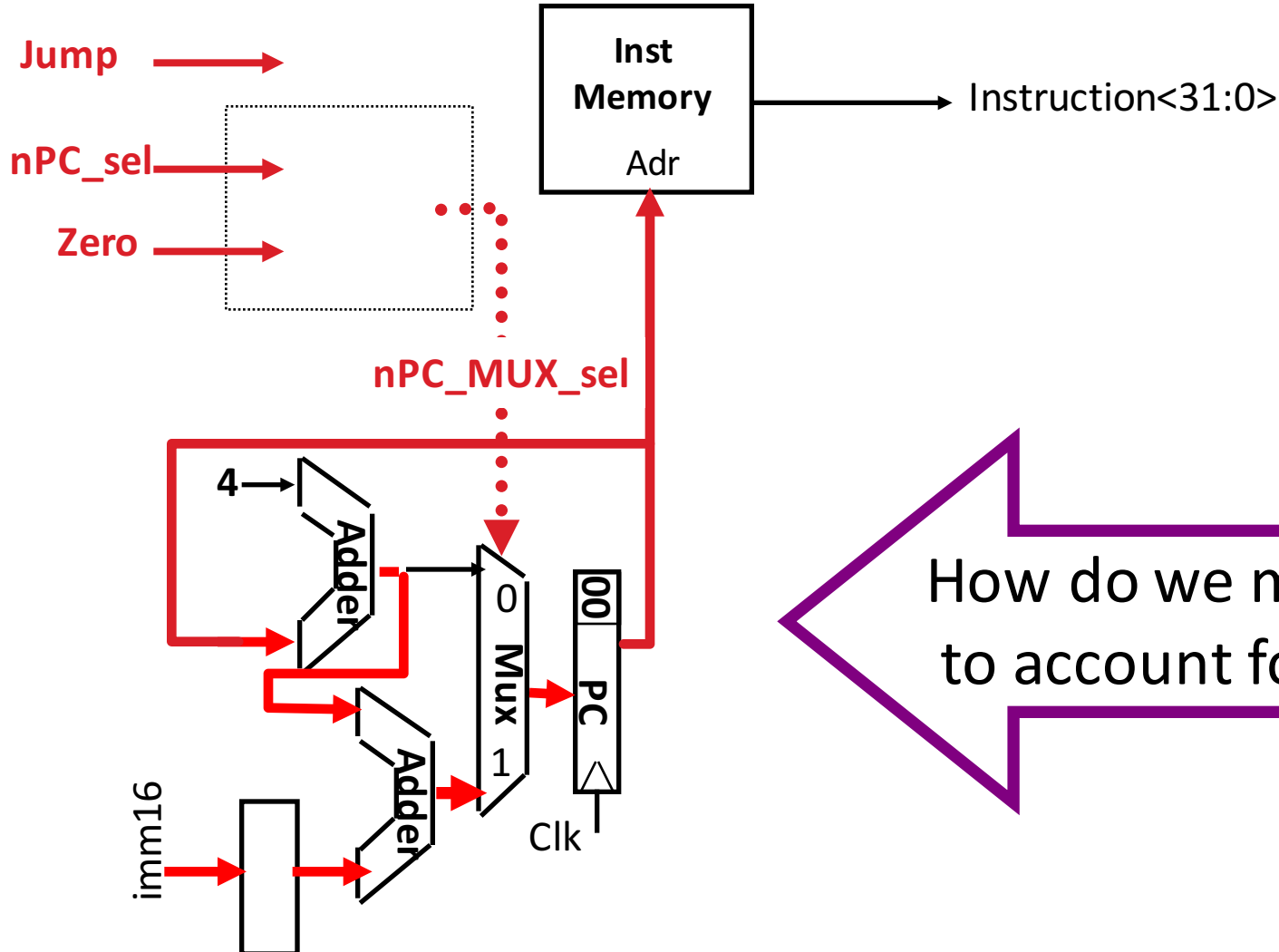- New PC = { PC[31..28], target address, 00 }




How do we modify this to account for jumps?

Instruction Fetch Unit at the End of Jump



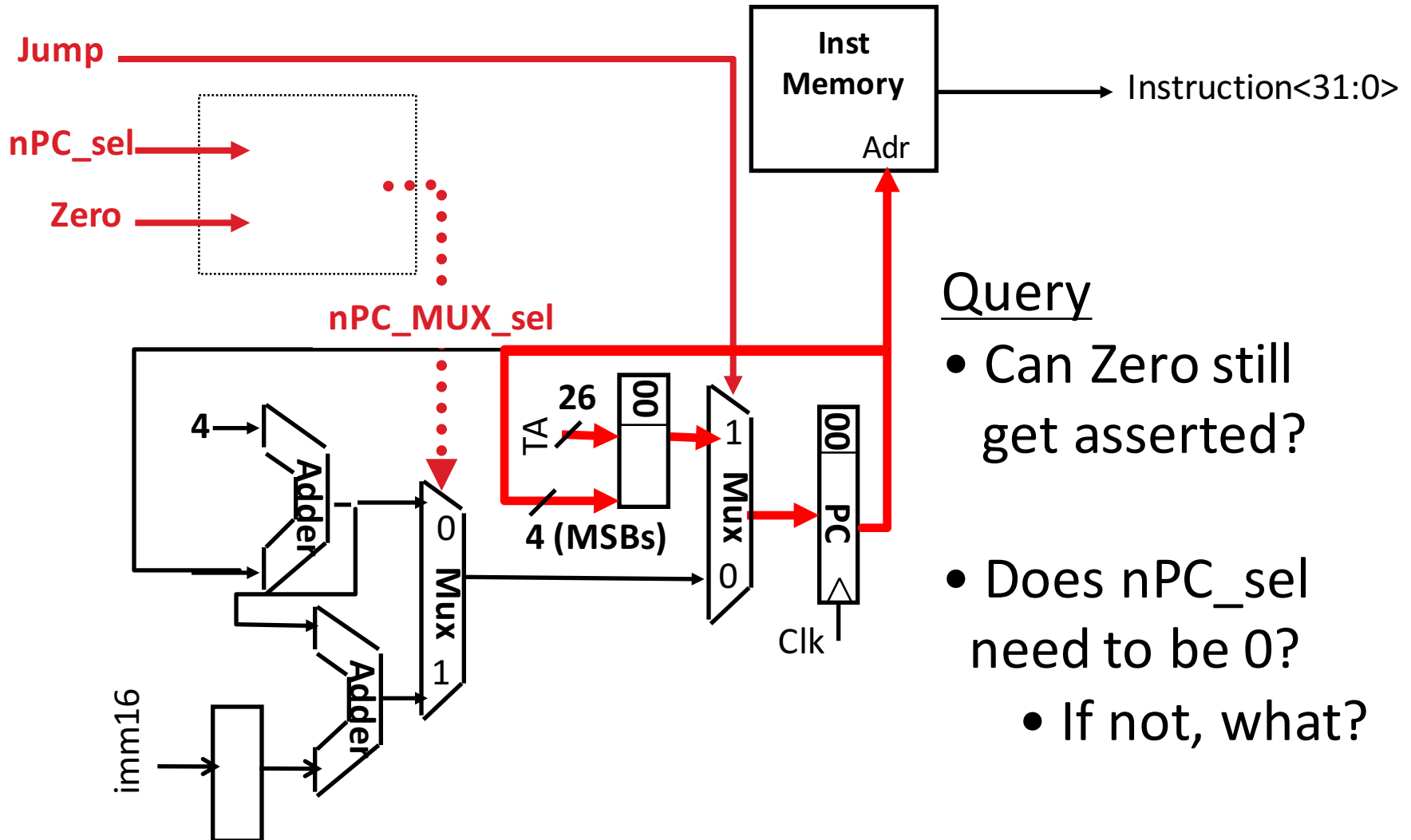- New PC = { PC[31..28], target address, 00 }



Query

- Can Zero still get asserted?
- Does nPC_sel need to be 0?
 - If not, what?